

**AMERICAN INTERNATIONAL
UNIVERSITY-BANGLADESH**

408/1, Kuratoli, Khilkhet, Dhaka 1229, Bangladesh



Assignment Title: Study of Combination of Series-Parallel Circuits and Verification of Δ -Y or Y- Δ Conversion Introduction.

Assignment No: 03

Date of Submission: October 23, 2022

Course Title: Introduction to Electrical Circuits Laboratory

Course Code: COE2102

Section: T

Semester: FALL **2022-23**

Course Teacher: BISHWAJIT BANIK PATHIK

Declaration and Statement of Authorship:

1. I/we hold a copy of this Assignment/Case-Study, which can be produced if the original is lost/damaged.
2. This Assignment/Case-Study is my/our original work and no part of it has been copied from any other student's work or from any other source except where due acknowledgement is made.
3. No part of this Assignment/Case-Study has been written for me/us by any other person except where such collaboration has been authorized by the concerned teacher and is clearly acknowledged in the assignment.
4. I/we have not previously submitted or currently submitting this work for any other course/unit.
5. This work may be reproduced, communicated, compared and archived for the purpose of detecting plagiarism.
6. I/we give permission for a copy of my/our marked work to be retained by the Faculty for review and comparison, including review by external examiners.
7. I/we understand that Plagiarism is the presentation of the work, idea or creation of another person as though it is your own. It is a form of cheating and is a very serious academic offence that may lead to expulsion from the University. Plagiarized material can be drawn from, and presented in, written, graphic and visual form, including electronic data, and oral presentations. Plagiarism occurs when the origin of them arterial used is not appropriately cited.
8. I/we also understand that enabling plagiarism is the act of assisting or allowing another person to plagiarize or to copy my/our work.

* Student(s) must complete all details except the faculty use part.

** Please submit all assignments to your course teacher or the office of the concerned teacher.

Group Name/No.: 8 / Ground

No	Name	ID	Program	Signature
1	LIDA KHAN MUKTI	22-47000-1	B. Sc. in CSE	Lida
2				
3				
4				
5				

Faculty use only

FACULTY COMMENTS

Marks Obtained

Total Marks

65

Abstract:

The main objective of this experiment was to analysis of simple DC series - parallel circuit. In doing so, we had to design an electrical circuit with relevant parameters and sources and set up the circuit with appropriate connections, sources and instruments. Then compared the measured value with the theoretical and simulation estimated value. For that, the series circuit can be solved using the Kirchoff's Voltage Law (KVL) and voltage divider rule (VDR). The parallel circuit can be solved using Kirchoff's current law (KCL) and current divider rule (CDR).

Theory:

- i) Series circuit: A circuit consist of any number of elements joined at terminal points, providing at least one closed path through which charge can flow. Two elements are in series if:
 - a) They have only one terminal in common (i.e., one lead of one is connected to only one lead of the other).
 - b) The common point between the two elements is not connected to another current-carrying element.

The current is the same through series elements. Total resistance of a series circuit is the sum of the resistance levels. In general, to find the total resistance of N resistors in series, the following equation is applied:

$$RT = R_1 + R_2 + R_3 + \dots + R_N \text{ (ohms)} \quad I = \frac{E}{RT} \text{ (Amperes)}$$

The voltage across each resistor (Figure 1) using Ohm's law; that is,

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3, \dots, V_N = IR_N \text{ (volts)}$$

$$\text{KVL}, E = V_1 + V_2$$

The voltage divider rule states that the voltage across a resistor in a series elements, and RT is the total resistance of series circuit, is equal to the value of that resistor times the total impressed voltage across the series elements divided by the total resistance of the series elements.

The following VDR equation is applied:

$$V_x = \frac{R_x E}{R_T} \text{ similarly, } V_1 = \frac{R_1 E}{R_T}, V_2 = \frac{R_2 E}{R_T}$$

where, V_x is the voltage across R_x , E is the impressed voltage across the series elements, and R_T is the total resistance of the series circuit.

ii) parallel circuit:

Two elements, branches, or networks are in parallel if they have two points in common. In general, to find the total resistance of N resistors in parallel, the following equation is applied:

$$\frac{1}{R_T} = \left(\frac{1}{R_1}\right) + \left(\frac{1}{R_2}\right) + \left(\frac{1}{R_3}\right) + \dots + \left(\frac{1}{R_N}\right) \text{ (ohms)}$$

The voltage across parallel elements is the same (Figure 2). ($V_1 = V_2 = E$)

$$I_1 = \frac{E}{R_1}, I_2 = \frac{E}{R_2} \text{ (Amperes)}$$

The current divider rule states that the current through any parallel branch is equal to the product of the total resistance of the parallel branches and the input current divided by the resistance of the branch through which the current is to be determined. The following CDR equation is applied:

$$I_x = \frac{R_T I}{R_x} \text{ similarly } I_1 = \frac{R_T I}{R_1}, I_2 = \frac{R_T I}{R_2}$$

Where, the input current I equal $\frac{V}{R_T}$, R_T is the total resistance of the parallel branches.

Substituting $V = I_x R_x$ into the above equation, I_x refers to the current through a parallel branch of resistance R_x .

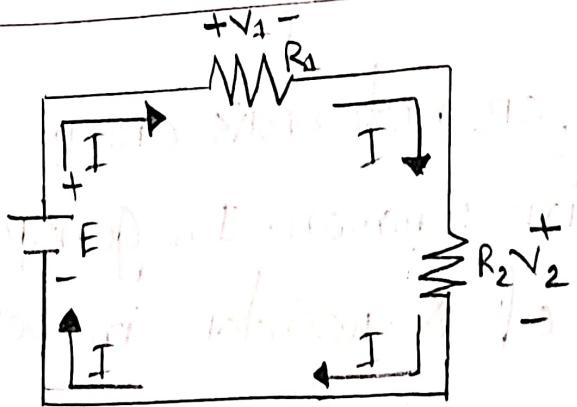


Figure 1: series circuit


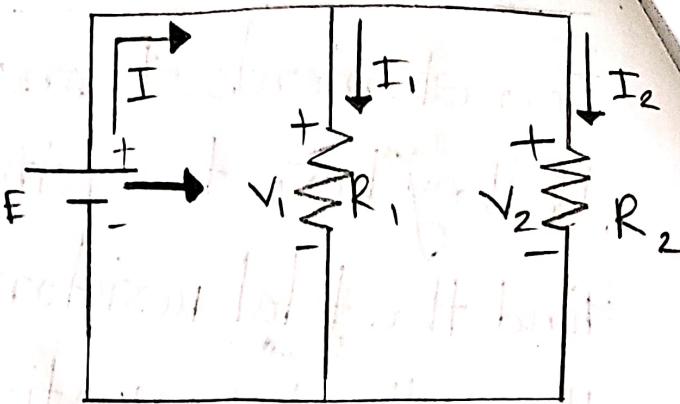


Figure 2: parallel circuit

Delta (Δ) and wye (Y) network: In many circuit applications, we encounter components connected together in one of two ways to form a three-terminal network: the "Delta" or Δ configuration, and the "Y" (also known as the "T") configuration.

wye (Y) network, Delta (Δ) network

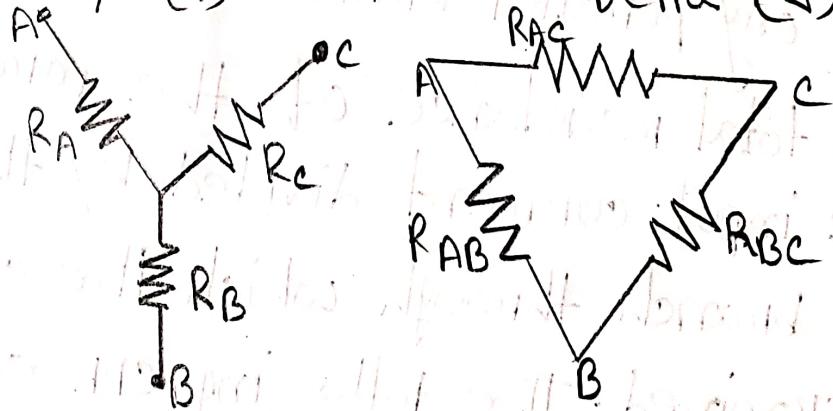

It is possible to calculate the proper values of resistors necessary to form one kind of network (Δ or Y) that behaves identically to the other kind, as analyzed from the terminal connections alone. That is, if we had two separate resistor networks, one Δ and one Y , each with its resistors hidden,

from view, with nothing but the three terminals. (A, B, and C) exposed for testing, the resistor could be sized for others. In other words, equivalent Δ and γ networks behave identically. There are several equations used to convert one network to the other.

To convert a Delta (Δ) to wye (γ)

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_C = \frac{R_{AC} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

To convert a wye (γ) to Delta (Δ)

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

$$R_{AC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

Apparatus:

1. Trainer Board

2. Avo meter or multimeter

3. DC source

4. Resistors

5. Connecting wires.

precautions: we've checked all the appatus were working properly or not. we implemented the circuit carefully where necessary. It was made sure that the voltmeter was connected in series through the resistor. we did not switch on the DC source while implementing the circuit in the trainer board.

Circuit Diagram:


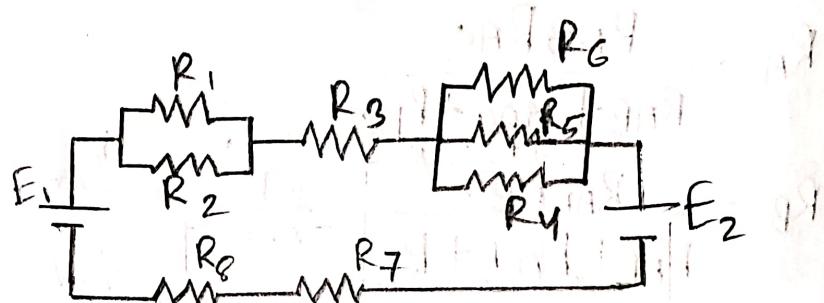


Figure 4

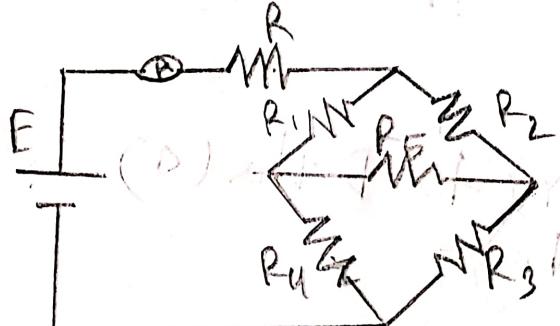

Data Table:

Figure 5

Table - 1 : Data table for series parallel connection

Calculated Value						Measured Value					
I (mA)	V _{R12} (mv)	V _{R3} (V)	V _{R456} (V)	V _{R7} (V)	V _{R8} (mv)	I (mA)	V _{R12} (mv)	V _{R3} (V)	V _{R456} (V)	V _{R7} (V)	V _{R8} (mv)
8.64×10^{-4}	44	0.28	0.11	0.48	87.2	8.59×10^{-4}	43	0.29	0.11	0.49	87.33

Table - 2: Data table for delta connection

VR	VR1	VR2	VR3	VR4	VR5	IR	IR1	IR2	IR3	IR4	IR5
6.801	0.58	1.72	2.521	1.43	1.211	2.03	1.2	0.756	0.53	1.47	0.66

Table - 3: Data table for wye connection

VR	VR1	VR2	VR6	VR7	VR8	IR	IR1	IR2	IR6	IR7	IR8
6.821	0.59	1.78	0.188	1.387	1.211	2.032	1.23	0.8	0.8	1.24	1.8

In figure 3,

$$\text{Given, } R_1 = 1\text{ k}\Omega = 1000\Omega$$

$$R_2 = 1\text{ k}\Omega = 1000\Omega$$

$$R_3 = 3.25\text{ k}\Omega = 3250\Omega$$

$$R_4 = 2\text{ k}\Omega = 2000\Omega$$

$$R_5 = 10\text{ k}\Omega = 10000\Omega$$

$$R_6 = 5\text{ k}\Omega = 5000\Omega$$

$$R_7 = 5.57\text{ k}\Omega = 5570\Omega$$

$$R_8 = 1\text{ k}\Omega = 1000\Omega$$

$$\text{Now, } R_{12} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{1000} + \frac{1}{1000} \right)^{-1} = 500\Omega$$

$$R_{456} = \left(\frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} \right)^{-1} = \left(\frac{1}{2000} + \frac{1}{10000} + \frac{1}{5000} \right)^{-1} = 1250\Omega$$

$$R_T = R_{12} + R_3 + R_{456} + R_7 + R_8$$

$$= 500 + 3250 + 1250 + 5570 + 1000 = 11570\Omega$$

$$\text{Then, } VR_{12} = \left(\frac{E + R_1}{R_T} \right) = \frac{10 + 500}{11570} = 0.0440V = 44mV$$

$$VR_3 = \frac{E + R_3}{R_T} = \frac{10 + 3250}{11570} = 0.2817V$$

$$VR_{U56} = \frac{E + R_{U56}}{R_T} = \frac{10 + 1250}{11570} = 0.1089V$$

$$VR_7 = \frac{E + R_7}{R_T} = \frac{10 + 5570}{11570} = 0.4822V$$

$$VR_8 = \frac{E + R_8}{R_T} = \frac{10 + 1000}{11570} = 0.0872V = 87.2mV$$

And,

$$I = \frac{E}{R_T} = \frac{10}{11570} = 8.64 \times 10^{-4} A$$

In figure 4,

$$\text{Given, } R = 3.357K$$

$$R_1 = 0.48K$$

$$R_2 = 2.221K$$

$$R_3 = 4.75K$$

$$R_4 = 0.973K$$

$$R_5 = 1.828K$$

$$(R_1 + R_2 + R_3 + R_4 + R_5) = (0.48 + 2.221 + 4.75 + 0.973 + 1.828) = 9.4K$$

32
And,

$$VR = 6.8V$$

$$VR_1 = 0.58V$$

$$VR_2 = 1.7V$$

$$VR_3 = 2.5V$$

$$VR_U = 1.43V$$

$$VR_5 = 1.2V$$

so, $IR = \frac{VR}{R} = \frac{6.8}{3.35} = 2.03mA$

$$IR_1 = \frac{VR_1}{R_1} = \frac{0.58}{0.48} = 1.2mA$$

$$IR_2 = \frac{VR_2}{R_2} = \frac{1.7}{2.221} = 0.765mA$$

$$IR_3 = \frac{VR_3}{R_3} = \frac{2.5}{4.75} = 0.53mA$$

$$IR_4 = \frac{VR_4}{R_4} = \frac{1.43}{0.973} = 1.47mA$$

$$IR_5 = \frac{VR_5}{R_5} = \frac{1.2}{1.828} = 0.66mA$$

A-Y conversion:

$$R_6 = \frac{(R_5 \times R_U)}{R_3 + R_U + R_5} = \frac{0.973 \times 1.828}{(4.75 + 0.973 + 1.828)} = 0.235k\Omega$$

$$R_7 = \frac{(R_5 \times R_3)}{R_3 + R_U + R_5} = \frac{0.75 \times 1.828}{(4.75 + 0.973 + 1.828)} = 1.12k\Omega$$

$$R_8 = \frac{(R_U \times R_3)}{R_3 + R_U + R_5} = \frac{1.43 \times 0.973}{(4.75 + 0.973 + 1.828)} = 0.596k\Omega$$

NOW,

$$VR = 6.821V$$

$$VR_1 = 0.59V$$

$$VR_2 = 1.78V$$

$$VR_6 = 0.188V$$

$$VR_7 = 1.387V$$

$$VR_8 = 1.211V$$

And,

$$IR = 2.032 \text{ mA}$$

$$IR_1 = 1.23 \text{ mA}$$

$$IR_2 = 0.8 \text{ mA}$$

$$IR_6 = 0.8 \text{ mA}$$

$$IR_7 = 1.24 \text{ mA}$$

$$IR_8 = 1.8 \text{ mA}$$

Result:

For Delta,

$$VR = 6.801V \text{ and } IR = 2.03 \text{ mA}$$

for wye,

$$VR = 6.821V \text{ and } IR = 2.032 \text{ mA}$$

Discussion: In this experiment we observed calculated series-parallel circuit. In the first circuit resistors were organised in series and parallel connection and current and voltages of different component were calculated. In the 2nd circuit the complicated network branchers were solved by converting the delta to Y connections. We solved the matter by following bread board connection rules. for measuring the current. Ammeter should be connected in series and voltmeter in parallel for voltage.

Conclusion: The whole experiment was about studying the series parallel circuit and verifying the Δ -Y conversion. Our experiment results fully support or verifies the Δ -Y conversion. In delta and Y connection we found the same amount of current which is enough to state experiment is accurate.

Reference:

1. Robert L. Boylestad, "Introductory Circuit Analysis", prentice Hall, 12th Edition, New York, 2010, ISBN 9780137146666.