

1. Design a system that can be used in a safety push button lock device. There will be two switches. If the value of A is greater than B or A is equal to B, lock mechanism opens. In any other case the lock mechanism remains closed. Let's say X is the lock mechanism, construct a truth table of the system and design the logic circuit for the system using magnitude comparator block diagram and necessary gate/s. [10]

Solution: In question it is given that, there will be two switches, which are A & B. Normal switches are only capable of being on or off at one time, never both at the same time. Because of this, we represent A & B as 1 bit numbers.

A	B	Condition	lock mechanism(X) logic output-
0	0	$A=B$ (lock opens)	1
0	1	$A < B$ (lock closed)	0
1	0	$A > B$ (lock opens)	1
1	1	$A=B$ (lock opens)	1


Truth table

(Ans)


	A	B	
	0	1	
0	1 <sup>0</sup>	0 <sup>1</sup>	
1	1 <sup>2</sup>	1 <sup>3</sup>	

K-map

$$\text{So, } X = A + \bar{B}$$

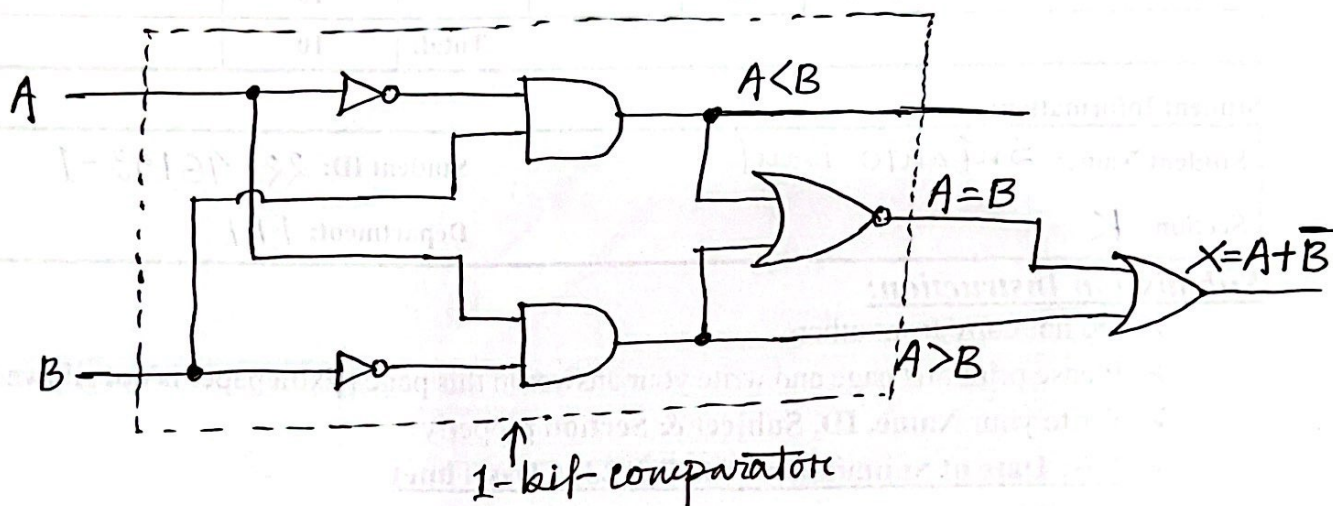


Now using block diagram →

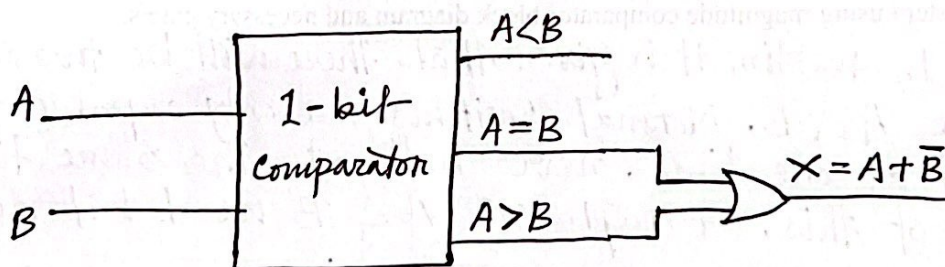

Design of the lock mechanism (X) logic circuit-  
using 1-bit-magnitude comparator block diagram  
(Ans)

Now using gates →

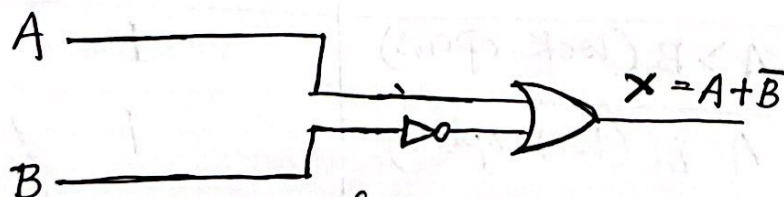

Design of the lock mechanism (X)  
using only gates. (Ans)