



American International University- Bangladesh (AIUB)
Faculty of Engineering (EEE)

Course Name :	Electronic Devices	Course Code :	EEE 2103
Semester :	Spring 2023	Sec : K	
POI	P.b.2.C4	Assignment No :	Non-OBE
Student Name:	Abir bokhtiar	Student ID:	22-47038-1
Submission Date:	25 April 2023	Due Date :	26 April 2023

Assignment Problem

- 1 **Analyze** the transfer characteristics curve of D-MOSFET and E-MOSFET (any one channel is ok) using the Shockley's equation and shorthand method. Consider the pinch-off voltage is [use appropriate sign here] [three digits before the last digit of your ID] mV and I_{DSS} is [three digits before the last digit of your ID] mA. [4]

Ans-to-the-ques-no-1

Given, $I_{DSS} = 38 \text{ mA}$

$V_{GS(th)} = +38 \text{ mV}$ for (E-mosfet) n-channel

$V_{GS(th)} = -38 \text{ mV}$ for (D-mosfet) n-channel

Here, assuming for the range upto 50 mV,

$$\begin{aligned} K &= \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2} \\ &= \frac{38 \text{ mA}}{(50 - 38)^2} \\ &= 0.26 \end{aligned}$$

For, Enhancement-mosfet,



When, $I_D = 0 \text{ mA}$, $V_{GS} = 38 \text{ mV}$

$$\begin{aligned} \text{when, } V_{GS} = 45 \text{ mV, } I_D &= K [V_{GS(on)} - V_{GS(th)}]^2 \\ &= 0.26 [45 - 38]^2 \end{aligned}$$

$$= 12.74 \text{ mA}$$


$$\begin{aligned} \text{when, } V_{GS} = 50 \text{ mV, } I_D &= K [V_{GS(on)} - V_{GS(th)}]^2 \\ &= 0.26 [50 - 38]^2 \\ &= 37.44 \text{ mA} \end{aligned}$$

V_{GS}	I_D
0	3.8 mA
-11.4 V	19 mA
-19 V	9.5 mA
-38 V	0

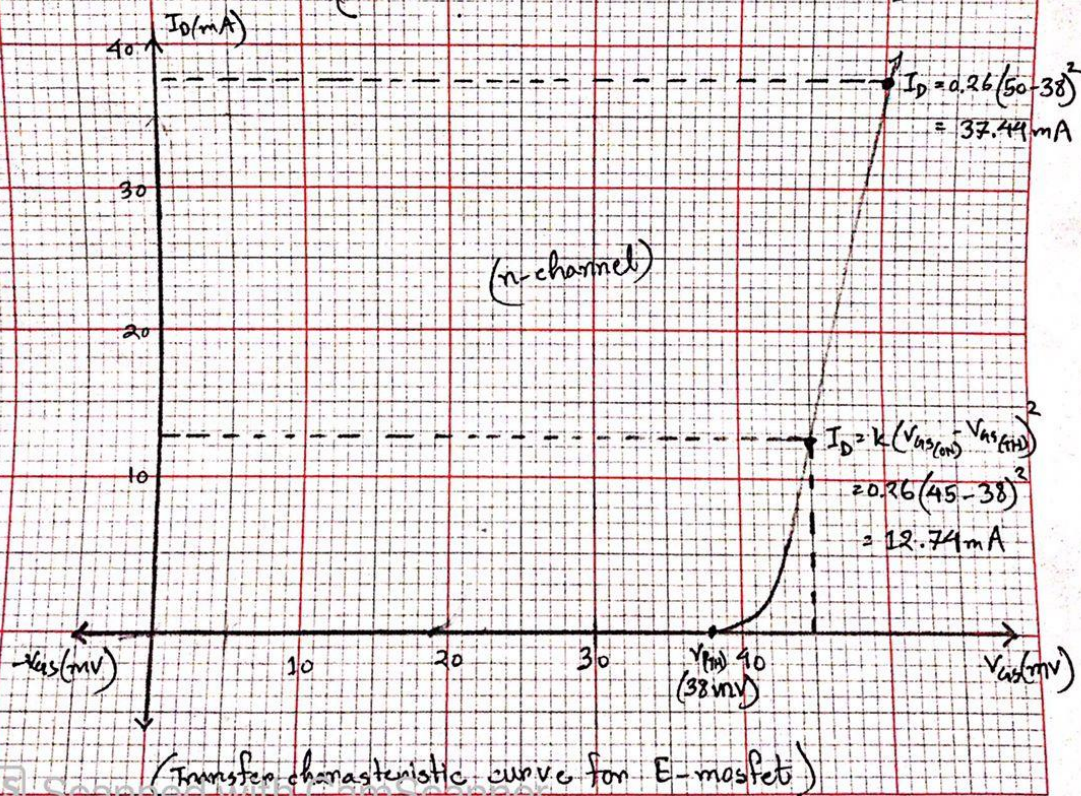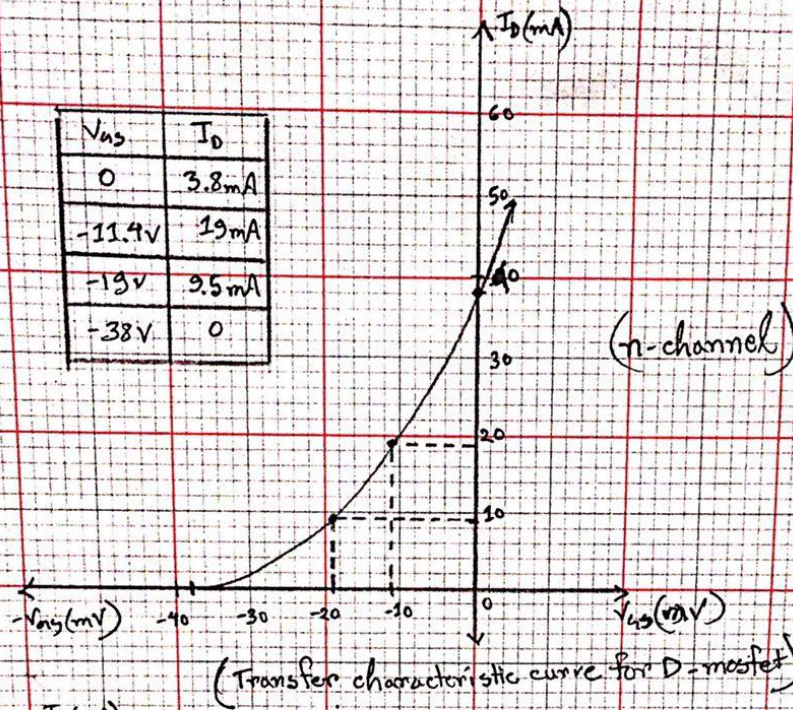

- 2 **Analyze** the Q points (I_{DQ} , V_{GSQ}) for different values of the R_s ($220\ \Omega$ and $770\ \Omega$) for the E-MOSFET voltage divider configuration given in Fig. 2. [4]

Figure for Question 2

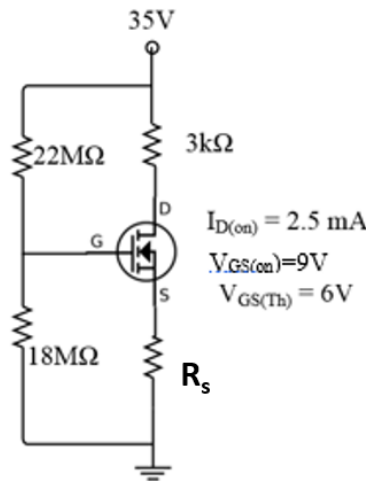

Ans-to-the-ques-no-2

Assuming that given device is working in saturation region,

$$k = \frac{I_{D(ON)}}{[V_{GS(ON)} - V_{GS(TH)}]^2} = \frac{2.5 \text{ mA}}{(9 - 6)^2} = 0.28 \text{ mA/V}^2$$

$$\text{Now, } I_D = k [V_{GS(ON)} - V_{GS(TH)}]^2 = 0.28 [V_{GS} - 6]^2 \text{ mA} \quad \text{--- (i)}$$

$$\text{And, } V_{GS} = V_G - V_S = V_G - I_D R_S \quad \text{--- (ii)}$$

Solving (i) & (ii),

$$V_{GS} = 15.75$$

$$\text{Using V.D.R, } V_G = \frac{18 \text{ M}\Omega}{18 \text{ M}\Omega + 22 \text{ M}\Omega} \times 35 \text{ V}$$

$$\therefore V_G = 15.75 \text{ V}$$

Solving (i) & (ii), For $R_S = 220 \Omega$

$$V_{GS} = 15.75 \text{ V} - (0.22 \text{ k}\Omega) \times [0.28 (V_{GS} - 6)^2]$$

$$\Rightarrow V_{GS} = 15.75 \text{ V} - (0.22 \text{ k}\Omega) \times (0.28) \times (V_{GS}^2 - 12 V_{GS} + 36)$$

$$\Rightarrow V_{GS} = 15.75 \text{ V} - (0.0616 V_{GS}^2 - 0.7392 V_{GS} + 2.2176)$$

$$\Rightarrow 0.0616 V_{GS}^2 + 0.2608 V_{GS} - 13.5324 = 0$$

$$\Rightarrow V_{GS} = 12.85 \text{ V} \& -17.088 \text{ V}$$

As V_{GS} should be greater than the threshold voltage in order for the MOSFET to be in on state, we consider, $V_{GS} = 12.85 \text{ V}$.

$$\therefore I_D = 0.28 [12.85 - 6]^2 = 13.14 \text{ mA}$$

For $R_S = 770 \Omega$,

$$V_{GS} = 15.75 \text{ V} - (0.77 \text{ k}\Omega) \times [0.28 (V_{GS} - 6)^2]$$

$$\Rightarrow V_{GS} = 15.75 \text{ V} - (0.2156) \times [V_{GS}^2 - 12V_{GS} + 36]$$

$$\Rightarrow V_{GS} = 15.75 \text{ V} - (0.2156 V_{GS}^2 - 2.5872 V_{GS} + 7.7616)$$


$$\Rightarrow 0.2156 V_{GS}^2 - 1.5872 V_{GS} - 7.9884 = 0$$


$$\text{Here, } V_{GS} = 10.8 \text{ V} \text{ \& } V_{GS} = -3.43 \text{ V}$$

$$\text{As } V_{GS} = 10.8 \text{ V} > V_{(TH)} = 6 \text{ V}$$

$$\therefore V_{GS} = 10.8 \text{ V}$$
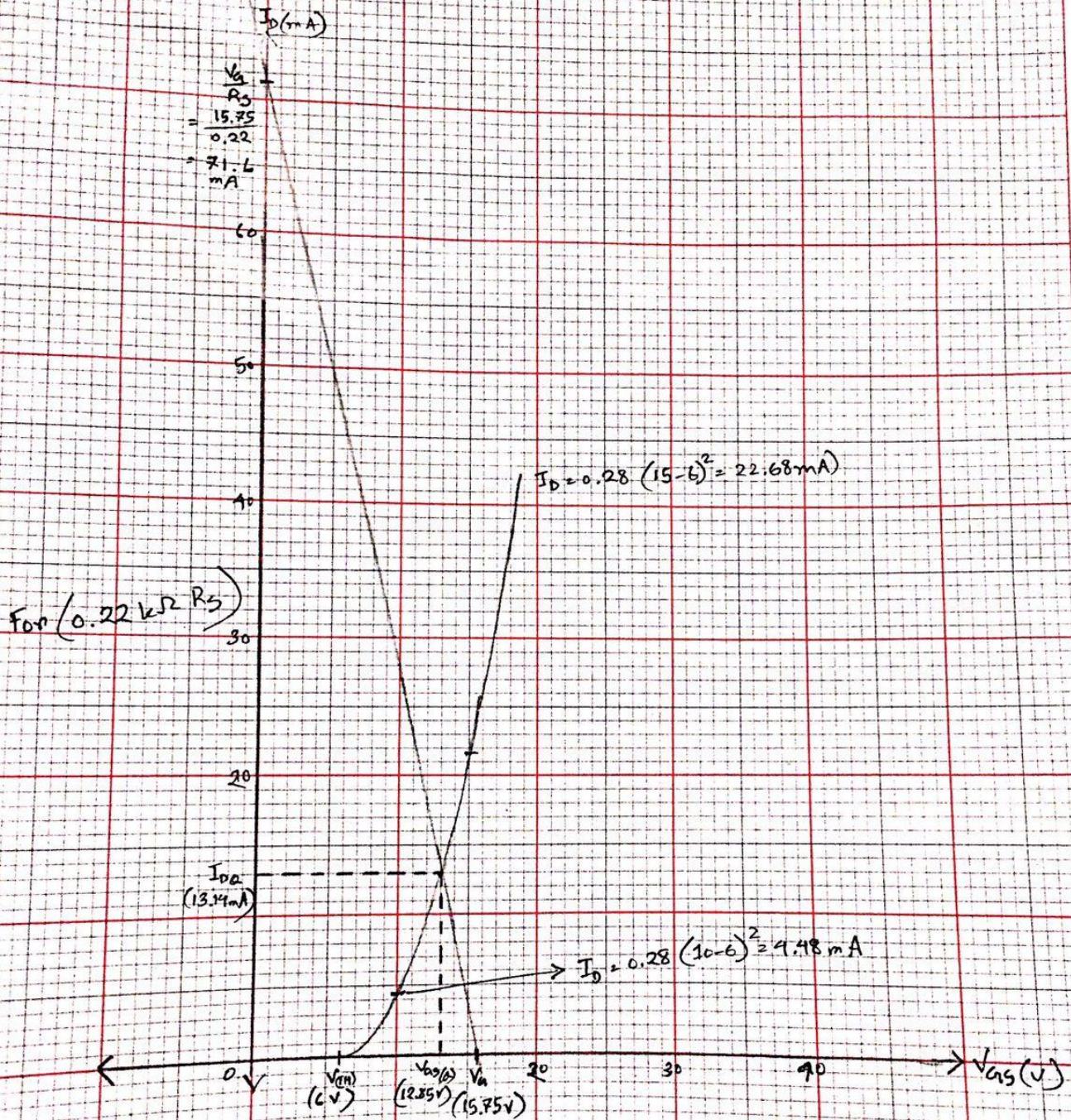
$$\text{Now, } I_D = 0.28 [10.8 - 6]^2 = 6.45 \text{ mA}$$



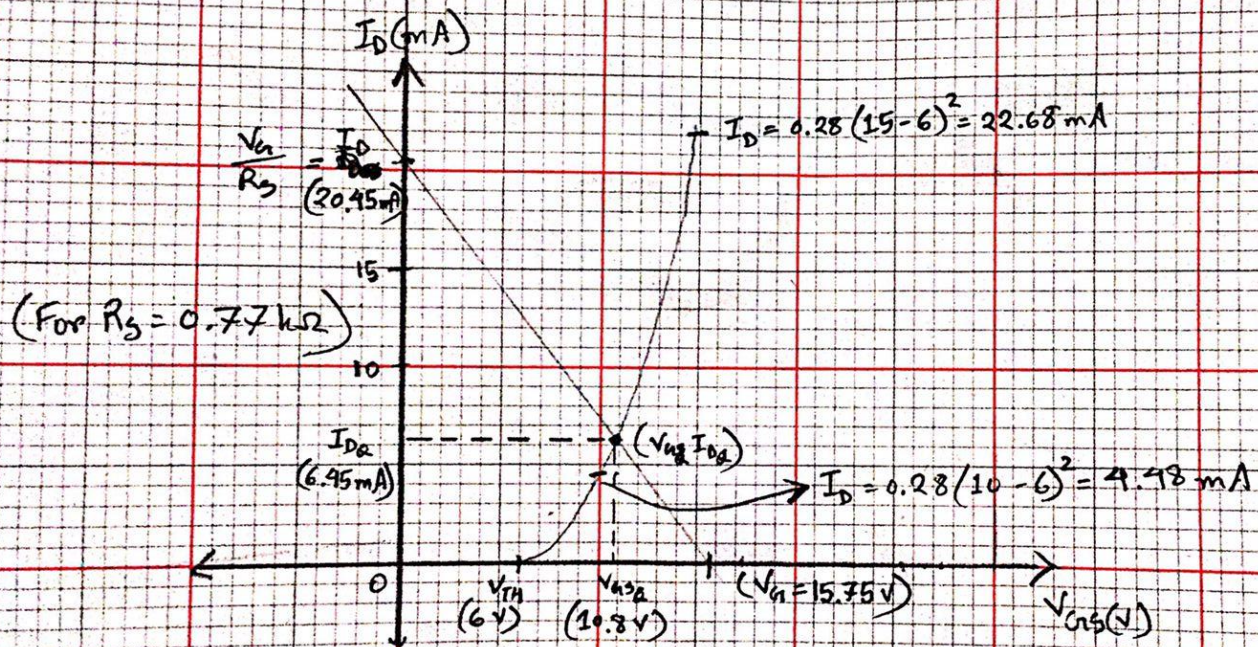

- 3 **Analyze** the g_m at different dc bias points of (-0.90 V, -1.40 V and -2.2 V) both graphically and mathematically for a JFET having I_{DSS} of 6 mA and $V_p = -5$ V and comment on it. [4]

Ans-to-the-ques-no-3

(Mathematical)

$$\text{Here, } g_{m0} = \frac{2 I_{DSS}}{|V_p|} = \frac{2 \times 6 \text{ mA}}{5 \text{ V}} = 2.4 \text{ mS}$$

$$\text{At } V_{GS} = -0.90 \text{ V,}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_p} \right] = 2.4 \text{ mS} \left[1 - \frac{-0.9}{-5} \right] = 1.968 \text{ mS}$$


$$\text{At } V_{GS} = -1.40 \text{ V,}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_p} \right] = 2.4 \text{ mS} \left[1 - \frac{-1.4}{-5} \right] = 1.728 \text{ mS}$$

$$\text{At } V_{GS} = -2.2 \text{ V,}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_p} \right] = 2.4 \text{ mS} \left[1 - \frac{-2.2}{-5} \right] = 1.344 \text{ mS}$$

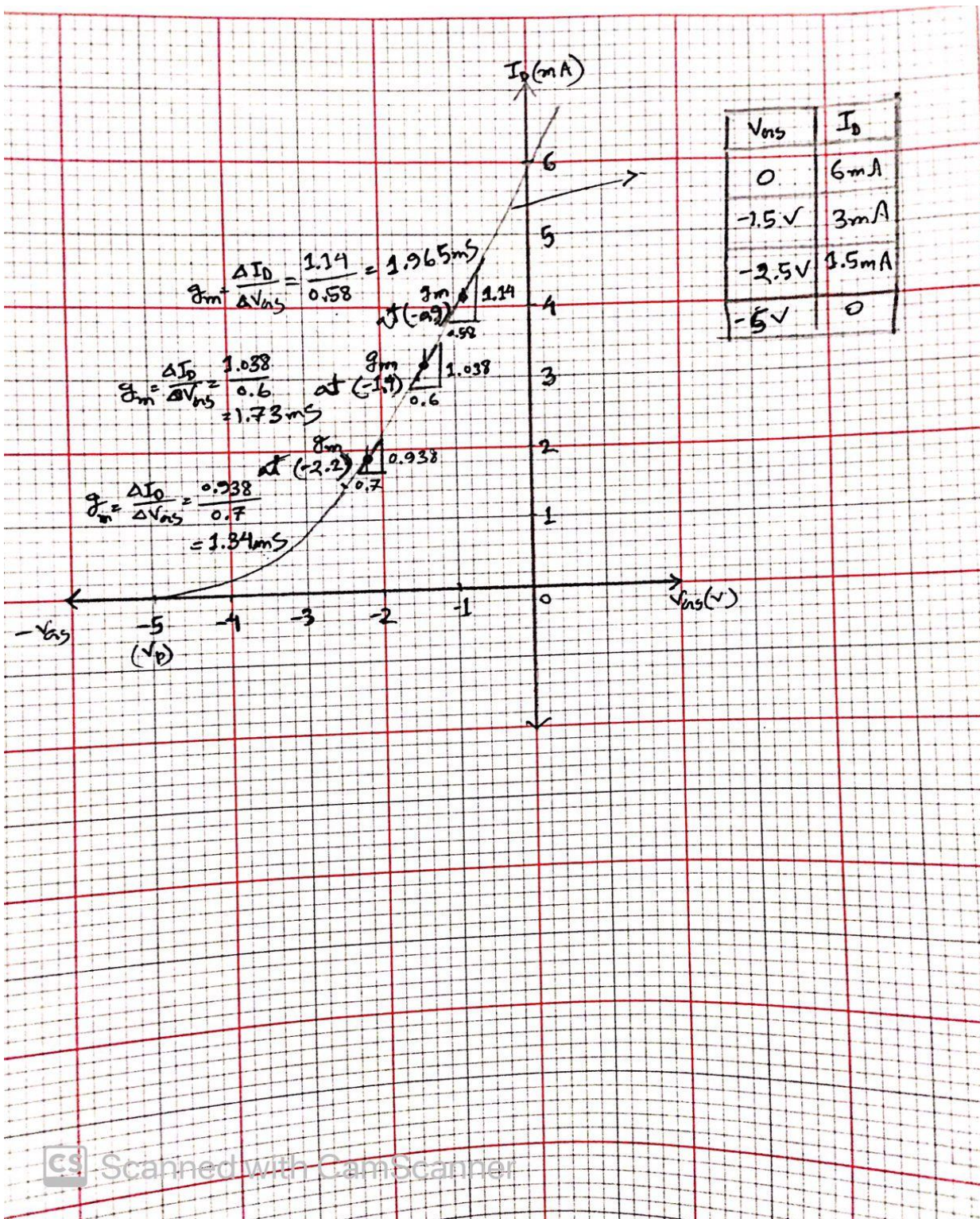The maximum value of g_m occurs when $V_{GS} = 0 \text{ V}$ and the minimum value at $V_{GS} = V_p$. The more negative the value of V_{GS} the less the value of g_m .



- 4 For the network given in Fig. 4, **analyze** A_v by determining the values Z_i , Z_o for $R_D = 3\text{ k}\Omega$ and $5\text{ k}\Omega$. [4]


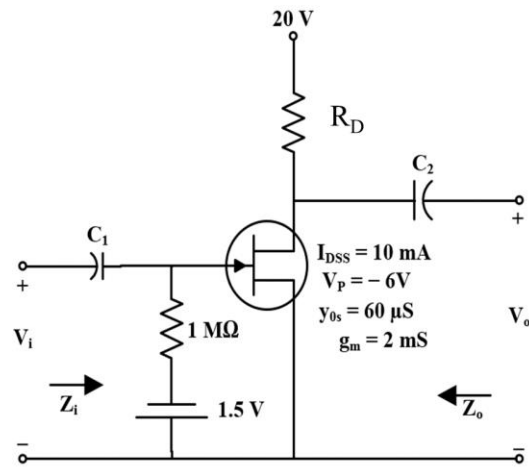


Figure for Question 4

Ans. to the ques. no. 4

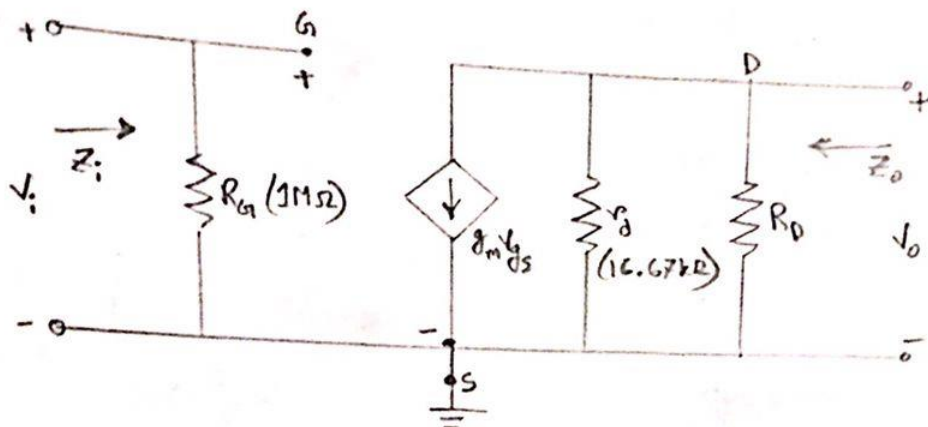

(JFET ac equivalent circuit)

Here, For $R_D = 3 \text{ k}\Omega$,

$$r_d \geq 10 R_D \\ \Rightarrow 16.67 \text{ k}\Omega \not\geq 10 \times 3 \text{ k}\Omega$$

$$r_d = \frac{1}{y_{os}} = \frac{1}{60 \mu\text{S}} = 16.67 \text{ k}\Omega$$

$$\therefore Z_i = R_G = 1 \text{ M}\Omega$$

$$\therefore Z_o = R_D \parallel r_d = (3 \parallel 16.67) \text{ k}\Omega = \left(\frac{1}{3} + \frac{1}{16.67} \right)^{-1} \text{ k}\Omega = 2.54 \text{ k}\Omega$$

Now, For $R_D = 5 \text{ k}\Omega$,

$$r_d \geq 10 R_D \Rightarrow 16.67 \text{ k}\Omega \not\geq 10 \times 5 \text{ k}\Omega$$

$$\therefore Z_i = R_G = 1 \text{ M}\Omega$$

$$\therefore Z_o = R_D \parallel r_d = (5 \parallel 16.67) \text{ k}\Omega = \left(\frac{1}{5} + \frac{1}{16.67} \right)^{-1} \text{ k}\Omega = 3.85 \text{ k}\Omega$$

$$\text{Now, } A_{v(3 \text{ k}\Omega)} = -g_m (R_D \parallel r_d) = -(2 \text{ mS})(2.54 \text{ k}\Omega) = -5.08$$

$$A_{v(5 \text{ k}\Omega)} = -g_m (R_D \parallel r_d) = -(2 \text{ mS})(3.85 \text{ k}\Omega) = -7.7$$

So, after analyzing voltage gain for $R_D = 3 \text{ k}\Omega$ and $5 \text{ k}\Omega$, we can say that, increase in drain resistance result in increase in voltage gain.

- 5 Design a self-bias network using a JFET transistor with $I_{DSS} = 10 \text{ mA}$ and $V_P = -4 \text{ V}$ to have a Q-point at $I_{DQ} = 6 \text{ mA}$ using a supply of 16 V . Assume that $R_D = 3R_S$ and use standard values. [4]

Ans-to-the-ques-no-5

Given, $I_{DSS} = 10 \text{ mA}$

$$V_P = -4 \text{ V}$$

$$I_{DQ} = 6 \text{ mA}$$

$$V_{CC} = 16 \text{ V}$$

$$R_D = 3R_S$$

From Shockley's eqⁿ,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\Rightarrow 6 \text{ mA} = 10 \text{ mA} \left(1 + \frac{V_{GS}}{4} \right)^2$$

$$\Rightarrow 1 + \frac{V_{GS}}{4} = \sqrt{\frac{6}{10}} \Rightarrow \frac{V_{GS}}{4} = \sqrt{\frac{6}{10}} - 1$$

$$\Rightarrow V_{GS} = \sqrt{\frac{16}{10}} \times 4 \times (-0.025)$$

$$\therefore V_{GS} = -0.9 \text{ V}$$

Using KVL, $V_{GS} = -I_D R_S$

$$\Rightarrow R_S = -\frac{V_{GS}}{I_D} = \frac{0.9 \text{ V}}{6 \times 10^{-3} \text{ A}}$$

$$\therefore R_S = 0.15 \text{ k}\Omega$$

$$\text{Now, } R_D = 3R_S = 0.45 \text{ k}\Omega$$

