

Electronic Devices

Final Term Lecture - 07

Reference book:

Electronic Devices and Circuit Theory (Chapter-7)

Robert L. Boylestad and L. Nashelsky , (11th Edition)



SELF-BIAS EXAMPLE Contd.

- Plot the **transfer curve** using I_{DSS} and V_P using shorthand method:

V_{GS}	I_D
0	I_{DSS}
$0.3V_P$	$I_{DSS}/2$
$0.5V_P$	$I_{DSS}/4$
V_P	0mA

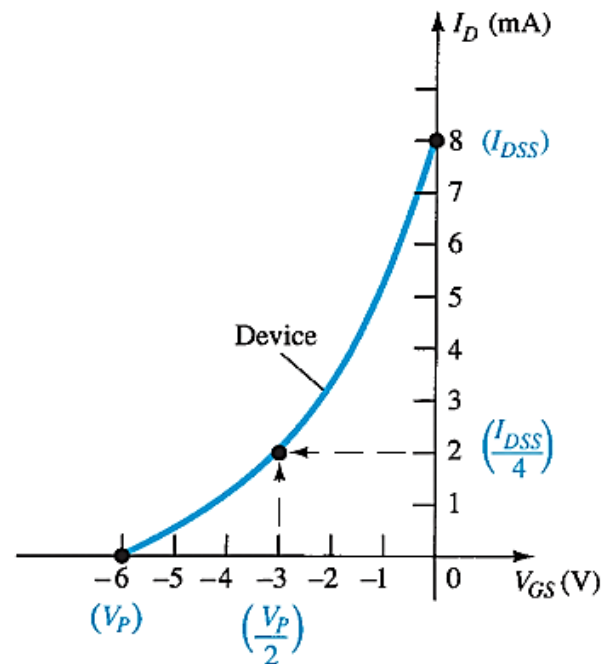


FIG. 7.14

Sketching the device characteristics for the JFET of Fig. 7.12.

 


FIG. 7.12

Example 7.2.

SELF-BIAS EXAMPLE Contd.

- Superimpose the **load line** on top of the **transfer curve**:

$$V_{GS_Q} = -2.6 \text{ V}$$

$$I_{D_Q} = 2.6 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_G = 0 \text{ V}$$

$$V_D = V_{DS} + V_S$$

$$V_D = V_{DD} - I_D R_D$$

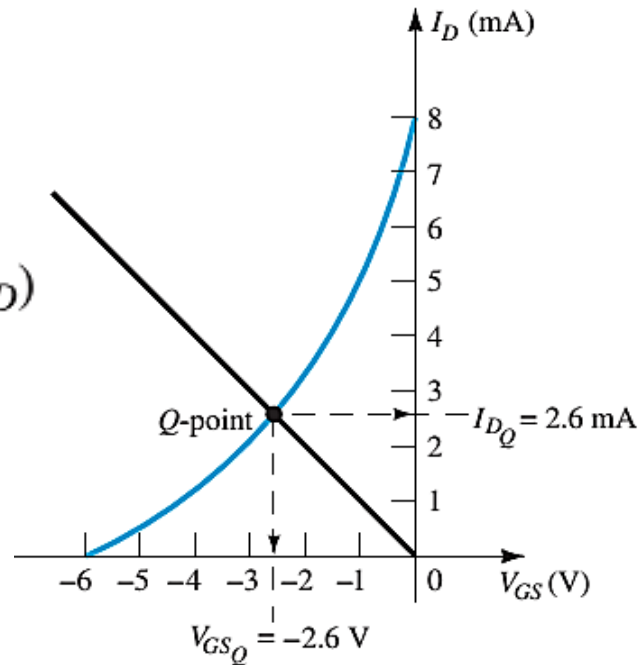


FIG. 7.15

Determining the Q -point for the network of Fig. 7.12.

 


FIG. 7.12

Example 7.2.

JFET: VOLTAGE-DIVIDER BIAS

- The source V_{DD} **was separated into two equivalent sources** to permit a further separation of the input and output regions of the network.
- Since $I_G = 0A$, Kirchoff's current law requires that $I_{R1} = I_{R2}$ and the series equivalent circuit appearing to the left of the figure can be used to find the level of V_G .

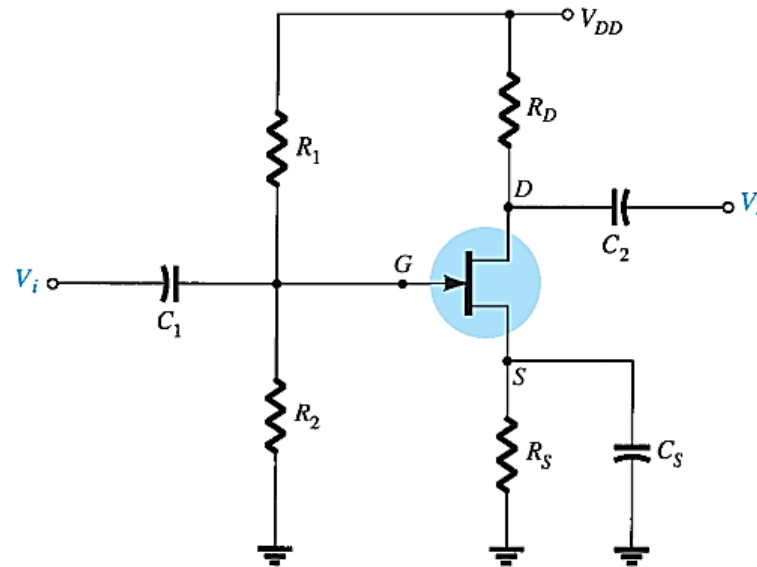


FIG. 7.17

Voltage-divider bias arrangement.

VOLTAGE-DIVIDER BIAS

- V_G can be found using the voltage divider rule:

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

- Using Kirchoff's Law on the input loop:

$$V_D = V_{DD} - I_D R_D$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_S = I_D R_S$$

$$V_{GS} = V_G - I_D R_S$$

- Rearranging and using $I_D = I_S$:

$$I_{R1} = I_{R2} = \frac{V_{DD}}{R_1 + R_2}$$

- Again the Q point needs to be established by plotting a line that intersects the transfer curve.

 


FIG. 7.18

Redrawn network of Fig. 7.17 for dc analysis.

VOLTAGE-DIVIDER BIAS

- **Graphical Approach** (to find V_{GSQ} and I_{DQ}):
 - Plot a line for:
 - » $V_{GS} = V_G$ when $I_D = 0A$
 - » $V_{GS} = 0V$ when $I_D = V_G/R_S$.
 - Plot the **transfer curve** using I_{DSS} and V_P using **shorthand method**.
 - The Q-point is located at the intersection.

V_{GS}	I_D
0	I_{DSS}
$0.3V_P$	$I_{DSS}/2$
$0.5V_P$	$I_{DSS}/4$
V_P	0mA

$$V_{GS} = V_G - I_D R_S$$

 


FIG. 7.19

Sketching the network equation for the voltage-divider configuration.

EFFECT OF INCREASING VALUES OF R_S

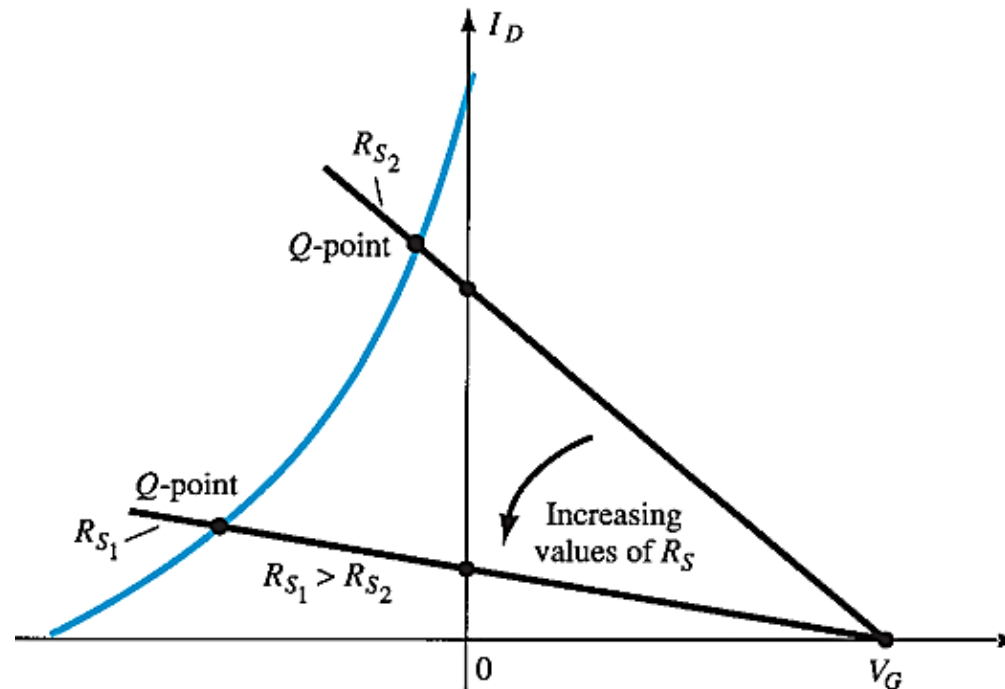


FIG. 7.20

Effect of R_S on the resulting Q-point.

JFET: VOLTAGE-DIVIDER BIAS EXAMPLE

- Determine I_{DQ} , V_{GSQ} , V_D , V_S , V_{DS} and V_{DG} .

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{GSQ} = -1.8V$$


$$I_{DQ} = 2.4mA$$

$$V_D = 10.24V$$

$$V_S = 3.6V$$

$$V_{DS} = 6.64V$$

$$V_{DG} = 8.24V$$

 

VOLTAGE-DIVIDER BIAS EXAMPLE Contd.

- **Graphical Approach** (to find V_{GSQ} and I_{DQ}):
 - Plot a line for:
 - » $V_{GS} = V_G$ when $I_D = 0A$
 - » $V_{GS} = 0V$ when $I_D = V_G/R_S$.
 - Plot the **transfer curve** using I_{DSS} and V_p using **shorthand method**.
 - Identify the Q-point.

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_S = I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DS} = V_D - V_S$$

$$V_D = V_{DD} - I_D R_D$$

$$V_{DG} = V_D - V_G$$

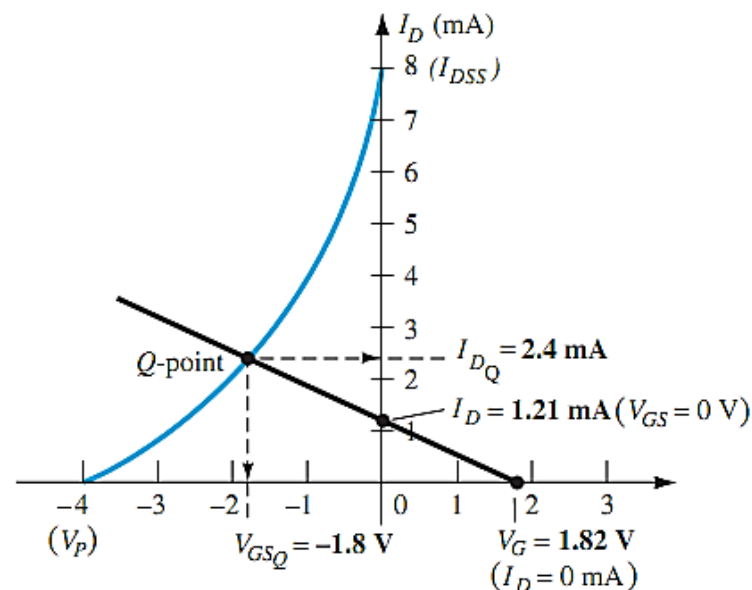


FIG. 7.22

Determining the Q-point for the network of Fig. 7.21.

D-MOSFET SELF-BIAS

- D-MOSFET bias circuits are **similar** to JFETs.
- The only **difference** is that D-MOSFETs can operate with **positive** values of V_{GS} and with I_D values that exceed I_{DSS} .

$$I_G \approx 0A$$

$$I_D = I_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

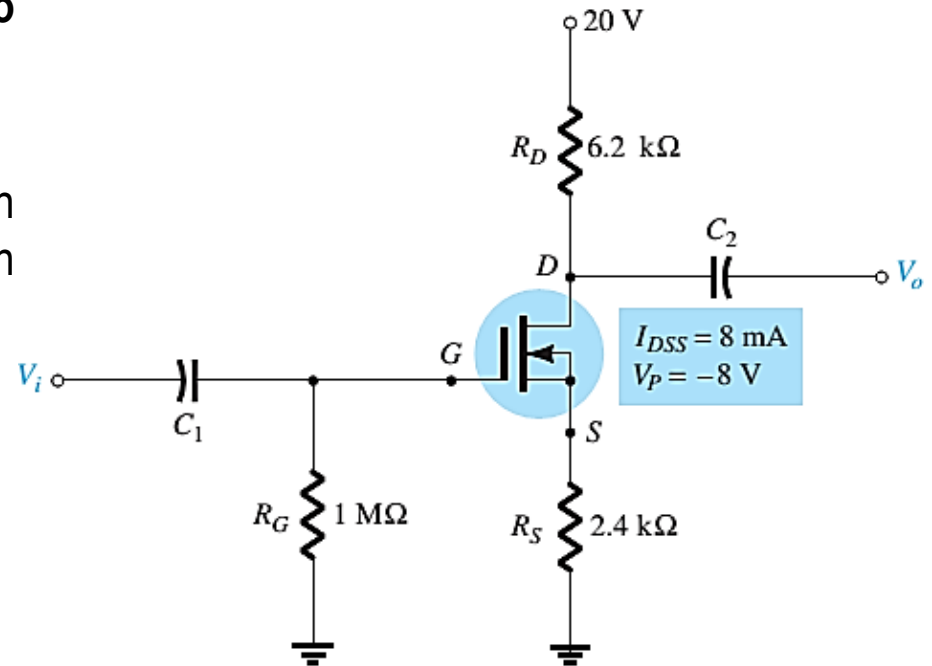


FIG. 7.33
Example 7.8.

D-MOSFET SELF-BIAS

- **Graphical Approach** (to find V_{GSQ} and I_{DQ}):


- Plot the **transfer curve** using I_{DSS} and V_P using **shorthand method**.

- Plot I_D vs V_{GS} using $V_{GS} = -I_D R_S$.

- Take a positive value of V_{GS} and find the I_D value using

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

 - The Q-point is located at the intersection.



D-MOSFET SELF-BIAS EXAMPLE

- Determine the I_{DQ} , V_{GSQ} and V_D .
- **Graphical Approach** (to find V_{GSQ} and I_{DQ}):
 - Plot the **transfer curve** using I_{DSS} and V_P using **shorthand method**.
 - Take a positive value of V_{GS} and find the I_D value using

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

- Plot I_D vs V_{GS} using $V_{GS} = -I_D R_S$.
- Identify the intersection Q-point.

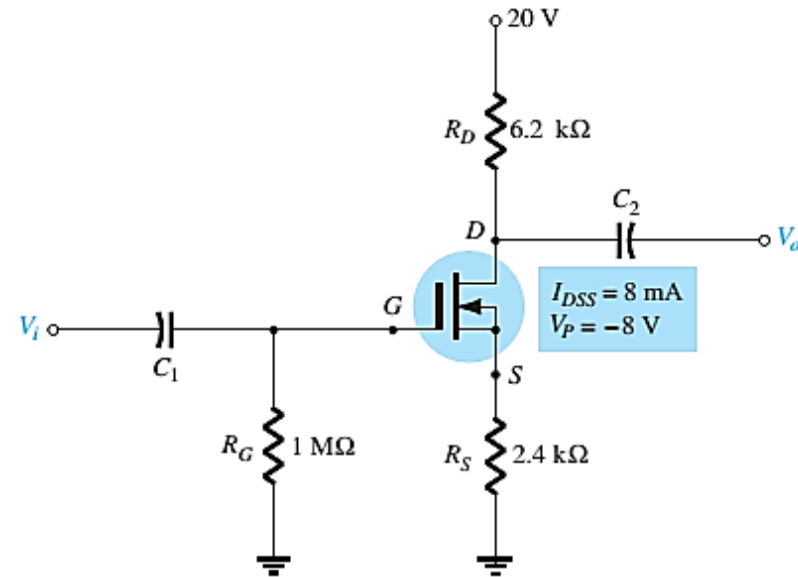


FIG. 7.33
Example 7.8.

D-MOSFET SELF-BIAS EXAMPLE

$$V_D = V_{DD} - I_D R_D$$


$$V_{GSQ} = -4.3 \text{ V}$$

$$I_{DQ} = 1.7 \text{ mA}$$

$$V_D = 9.46 \text{ V}$$

$$I_D = -\frac{V_{GS}}{R_S}$$
 
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$



D-MOSFET VOLTAGE-DIVIDER BIAS

- D-MOSFET bias circuits are similar to **JFETs**.

$$I_G \approx 0A$$

$$I_D = I_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

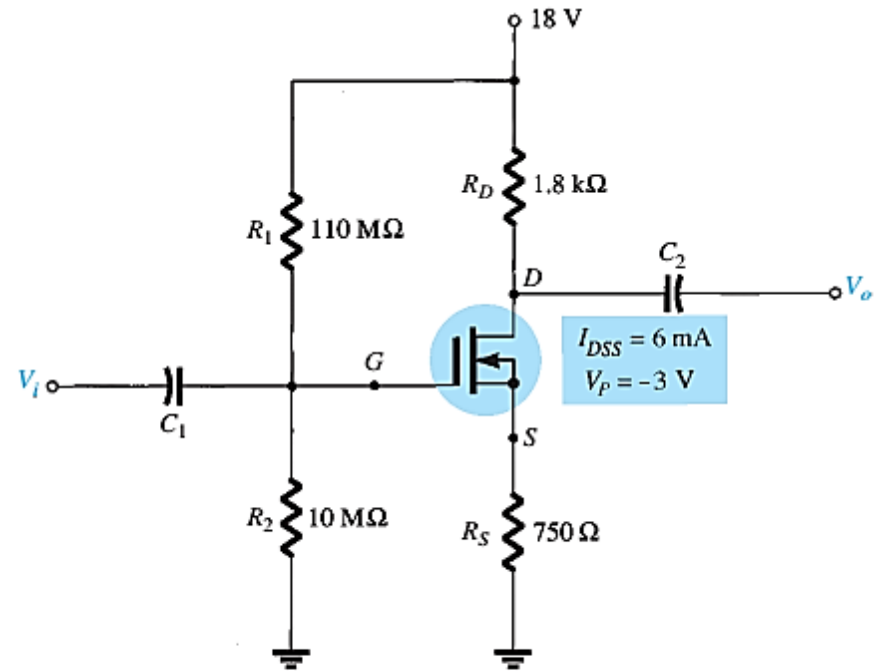


FIG. 7.30
Example 7.6.

D-MOSFET VOLTAGE-DIVIDER BIAS

- **Graphical Approach** (to find V_{GSQ} and I_{DQ}):

- Plot the **transfer curve** using I_{DSS} and V_P using **shorthand method**.
- Take a positive value of V_{GS} and find the I_D value using

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

- Plot I_D vs V_{GS} using $V_{GS} = V_G - I_D R_S$.
- The Q-point is located at the intersection.

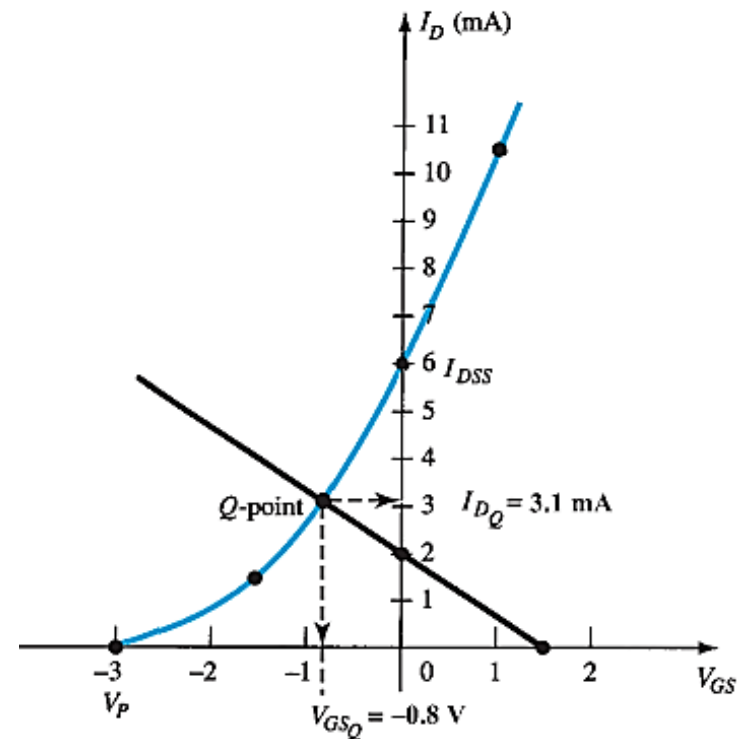


FIG. 7.31

Determining the Q-point for the network of Fig. 7.30.

End of Lecture-7

