
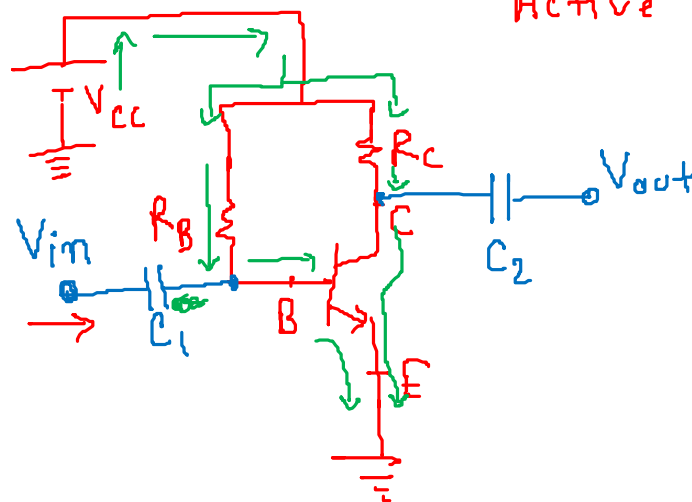


CE

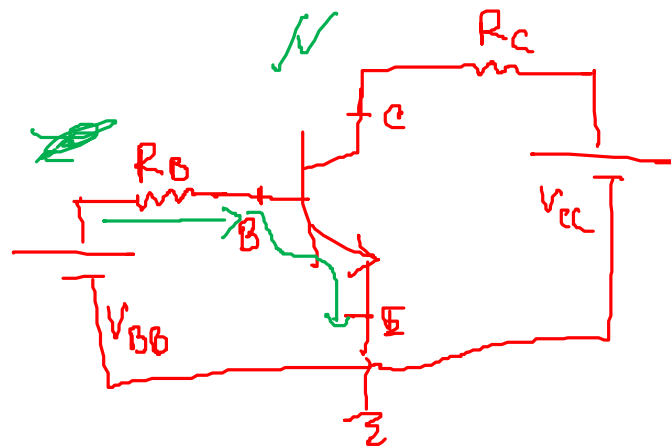

Active Region \rightarrow Amplifier
 \downarrow
 AC Signal

$$I_c = \beta I_B$$

$$\therefore \beta = \frac{I_c \rightarrow \text{o/p}}{I_B \rightarrow \text{i/p}}$$

$$X_c = \frac{1}{2\pi f C}$$

$$\text{DC} \cdot X_c = \frac{1}{0} = \infty (\Omega)$$

$$\text{DC: } E = 10V$$

$$T = \infty$$

$$f = \frac{1}{T} = 0$$



DC \rightarrow Cap $\rightarrow \infty (\Omega)$



$I_{dc} = 0 \text{ Amp (open)}$
 \downarrow
 Cap

$C_1, C_2 \rightarrow$ Coupling Capacitor

FIXED-BIAS CONFIGURATION

$C_1 \rightarrow C_p$: open

$$V_{BE} = 0.7V$$

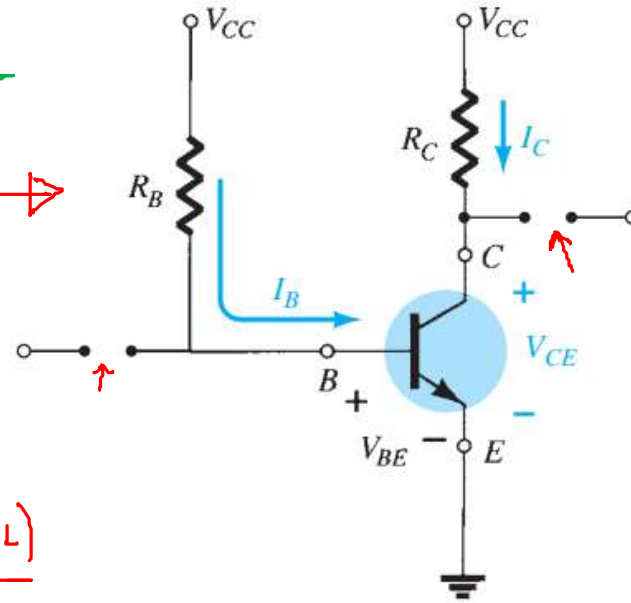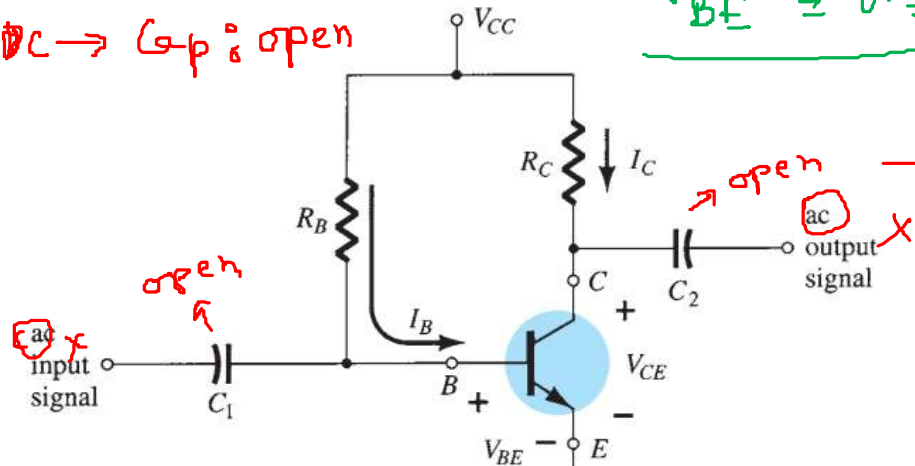


I/P (KVL)


$$+V_{CC} - I_B R_B - V_{BE} = 0$$

O/P (KVL)

$$+V_{CC} - I_C R_C - V_{CE} = 0$$

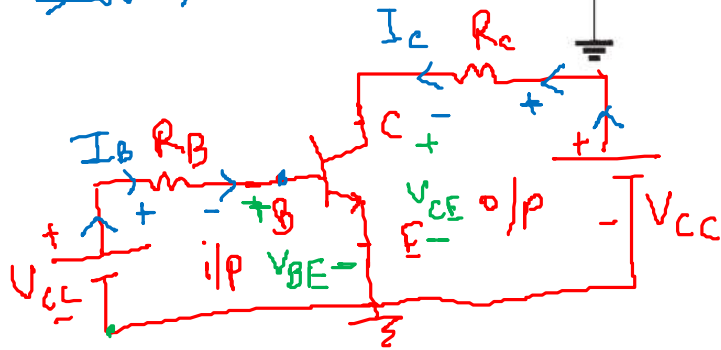

EXAMPLE 4.1

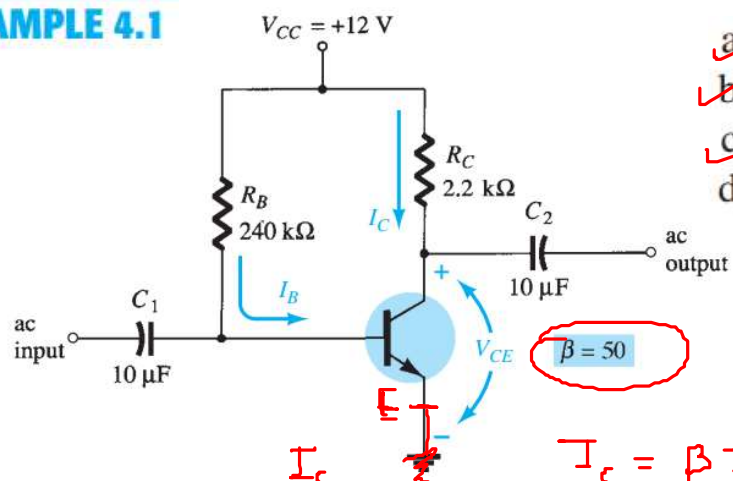

- a. I_{BQ} and I_{CQ} .
- b. V_{CEQ} .
- c. V_B and V_C .
- d. V_{BC} .

c) $V_E \Rightarrow$ Emitter to Ground

$$\frac{1}{\equiv} \longleftrightarrow \frac{1}{\equiv} \text{ diff } = 0$$

$$V_E = 0V$$

$$V_{BE} = 0.7 \Rightarrow V_B - V_E = 0.7 \therefore V_B = 0.7V$$

$$V_{CE} = 6.83 \Rightarrow V_C - V_E = 6.83 \therefore V_C = 6.83V$$

$$d) V_{BC} = V_B - V_C$$

$$= 0.7 - 6.83$$

$$= -6.13V$$

negative sign revealing that the junction is reversed-biased,

$$I_C = \beta I_B = 50 \times 0.047 = 2.35 \text{ mA}$$

$$b) V_{CC} - I_C R_C - V_{CE} = 0$$

$$\begin{aligned} \therefore V_{CE} &= V_{CC} - I_C R_C \\ &= 12 - 2.35 \times 2.2 \\ &= 6.83V \end{aligned}$$

$$a) V_{CC} - I_B R_B - V_{BE} = 0$$

$$\begin{aligned} \therefore I_B &= \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.7}{240} = 0.047 \text{ mA} \\ &= 47 \mu A \end{aligned}$$

EXAMPLE 4.2 Determine the saturation level

$$I_{C_{sat}} = \frac{V_{CC}}{R_C} = \frac{12 \text{ V}}{2.2 \text{ k}\Omega} = 5.45 \text{ mA}$$

Effect of β variation on the response of the fixed-bias configuration of Fig. 4.7.

β	$I_B (\mu A)$	$I_C (mA)$	$V_{CE} (V)$
→ 50	47.08	2.35	6.83 → Example 4.1
→ 100	47.08	4.71	1.64

The BJT collector current is seen to change by 100% due to the 100% change in the value of β . The value of I_B is the same, and V_{CE} decreased by 76%.

STABILITY

$$\% \text{ of } V_{CE} = \frac{6.83 - 1.64}{6.83} \times 100 = 76\%$$

Effect of β variation on the response of the emitter-bias configuration of Fig. 4.23.


β	$I_B (\mu A)$	$I_C (mA)$	$V_{CE} (V)$
50	40.1	2.01	13.97 → Example 4.4
100	36.3	3.63	9.11

$$\% \text{ of } V_{CE} = \frac{13.97 - 9.11}{13.97} \times 100\% = 34.78\% \approx 35\%$$



Now the BJT collector current increases by about 81% due to the 100% increase in β . Notice that I_B decreased, helping maintain the value of I_C —or at least reducing the overall change in I_C due to the change in β . The change in V_{CE} has dropped to about 35%. The network of Fig. 4.23 is therefore more stable than that of Fig. 4.7 for the same change in β .

EMITTER-BIAS CONFIGURATION

The dc bias network of Fig. 4.17 contains an emitter resistor to improve the stability level over that of the fixed-bias configuration. The more stable a configuration, the less its response will change due to undesireable changes in temperature and parameter

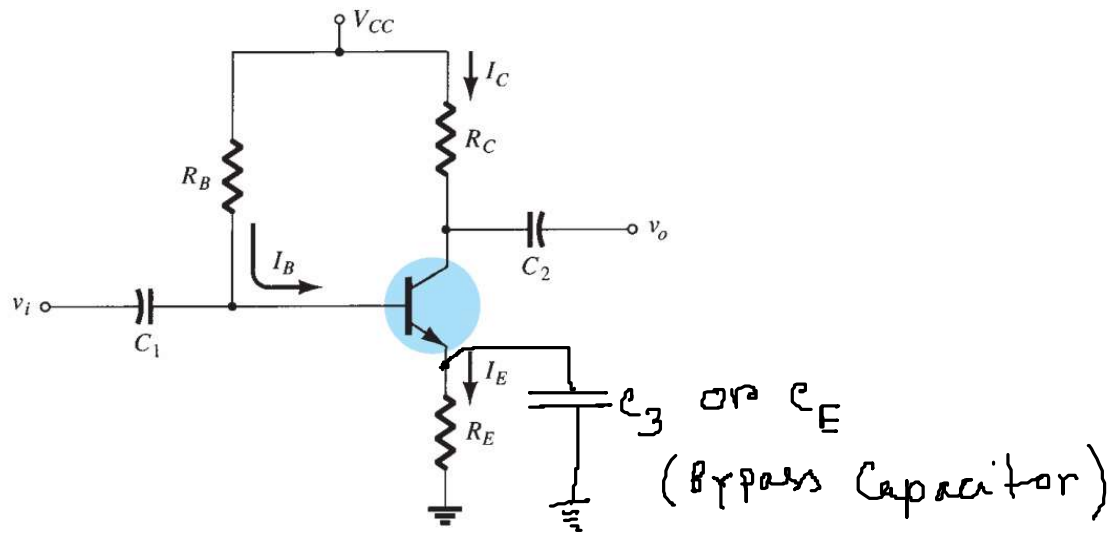

EXAMPLE 4.4

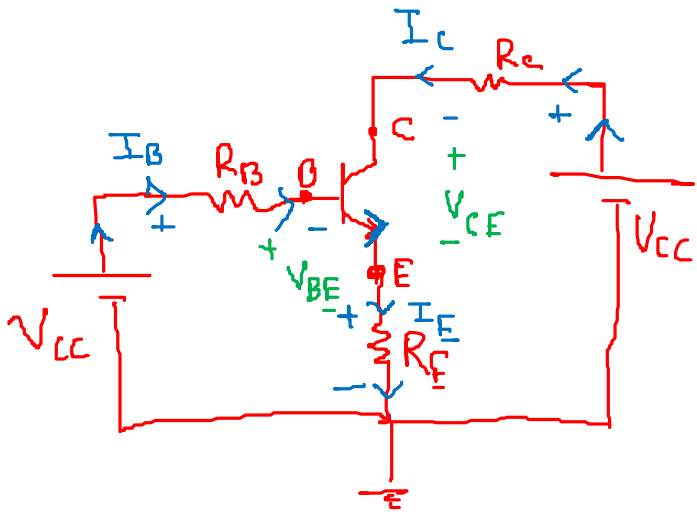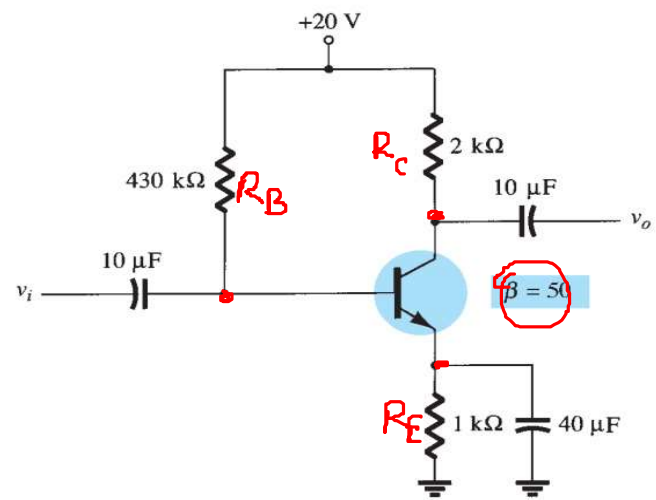

- a. I_B
- b. I_C
- c. V_{CE}
- d. V_C
- e. V_E
- f. V_B
- g. $V_{BC} = V_B - V_C = -19.21V$

c) $V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$

$\therefore V_{CE} = V_{CC} - I_C R_C - I_E R_E$
 $= V_{CC} - I_C R_C - I_C R_E$
 $= V_{CC} - I_C (R_C + R_E)$
 $= 20V - 2.01mA (2k\Omega + 1k\Omega)$
 $= 13.97V$

or $I_E = (1 + \beta) I_B$
 $I_E = I_B + I_C$
 $I_E \approx I_C$

a) $+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$

d) $V_{CE} = V_C - V_E$
 $\therefore V_C = V_{CE} + V_E$
 $= 13.97V + 2.01V = 15.98V$

$\Rightarrow V_{CC} - I_B R_B - V_{BE} - (1 + \beta) I_B R_E = 0$

e) $V_E = I_E R_E$
 $= I_C R_E$
 $= 2.01V$

$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) R_E}$
 $= 0.0401mA$
 $= 40.1\mu A$

f) $V_{BE} = V_B - V_E$
 $\therefore V_B = V_{BE} + V_E$
 $= 2.71V$

b) $I_C = \beta I_B = 2.01mA$

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E}$$