

AMERICAN INTERNATIONAL UNIVERSITY-BANGLADESH

408/1, Kuratoli, Khilkhet, Dhaka 1229, Bangladesh



Assignment Title: Study of Thevenin's Theorem and Maximum Power Transfer Theorem.

Assignment No: 05

Date of Submission: November 06, 2022

Course Title: Introduction to Electrical Circuits Laboratory

Course Code: COE2102

Section:

T

Semester: FALL

2022-23

Course Teacher:

BISHWAJIT BANIK PATHIK

Declaration and Statement of Authorship:

1. I/we hold a copy of this Assignment/Case-Study, which can be produced if the original is lost/damaged.
2. This Assignment/Case-Study is my/our original work and no part of it has been copied from any other student's work or from any other source except where due acknowledgement is made.
3. No part of this Assignment/Case-Study has been written for me/us by any other person except where such collaboration has been authorized by the concerned teacher and is clearly acknowledged in the assignment.
4. I/we have not previously submitted or currently submitting this work for any other course/unit.
5. This work may be reproduced, communicated, compared and archived for the purpose of detecting plagiarism.
6. I/we give permission for a copy of my/our marked work to be retained by the Faculty for review and comparison, including review by external examiners.
7. I/we understand that Plagiarism is the presentation of the work, idea or creation of another person as though it is your own. It is a form of cheating and is a very serious academic offence that may lead to expulsion from the University. Plagiarized material can be drawn from, and presented in, written, graphic and visual form, including electronic data, and oral presentations. Plagiarism occurs when the origin of them material used is not appropriately cited.
8. I/we also understand that enabling plagiarism is the act of assisting or allowing another person to plagiarize or to copy my/our work.

* Student(s) must complete all details except the faculty use part.

** Please submit all assignments to your course teacher or the office of the concerned teacher.

Group Name/No.: 8 / Ground

No	Name	ID	Program	Signature
1	MD. SHOHANUR RAHMAN SHOHAN	22-46013-1	B. Sc. in CSE	Shohan
2	MAHNAZ TABASSUM ORPITA	22-46024-1	B. Sc. in CSE	Orpita
3	LIDA KHAN MUKTI	22-47000-1	B. Sc. in CSE	Lida
4	TARIN SULTANA	22-47045-1	B. Sc. in CSE	Tarin
5	A. F. M. RAFIUL HASSAN	22-47048-1	B. Sc. in CSE	

Faculty use only

FACULTY COMMENTS	Marks Obtained	Total Marks

Assignment/Case-Study Cover; © AIUB-2020

Title : Study of Thevinin's Theorem and Maximum Power Transfer Theorem.

Abstract:

The experiment was conducted to investigate the study of Thevin's theorem and maximum power transfer theorem.

The objectives of this experiment are to find the Thevinin equivalent circuit, measure the load voltage and load current from given network also verify the maximum power transfer theorem. In this experiment, some basic tools like trainer board, voltmeter, ammeter, AVO meter or multimeter, DC source, resistors etc are used. By completing this experiment, we are able to develop the understanding of the Thevinin theorem and also justify the maximum power transfer theorem.

Theory:

Thevinin's Theorem: The Thevinin Theorem is a process of reducing complex circuit to an equivalent circuit which is consist of a single voltage source V_{TH} , a series resistance R_{TH} and a load resistance R_L . After that creating the Thevinin equivalent circuit, we may the

easily determine the load voltage V_L and the load current I_L .

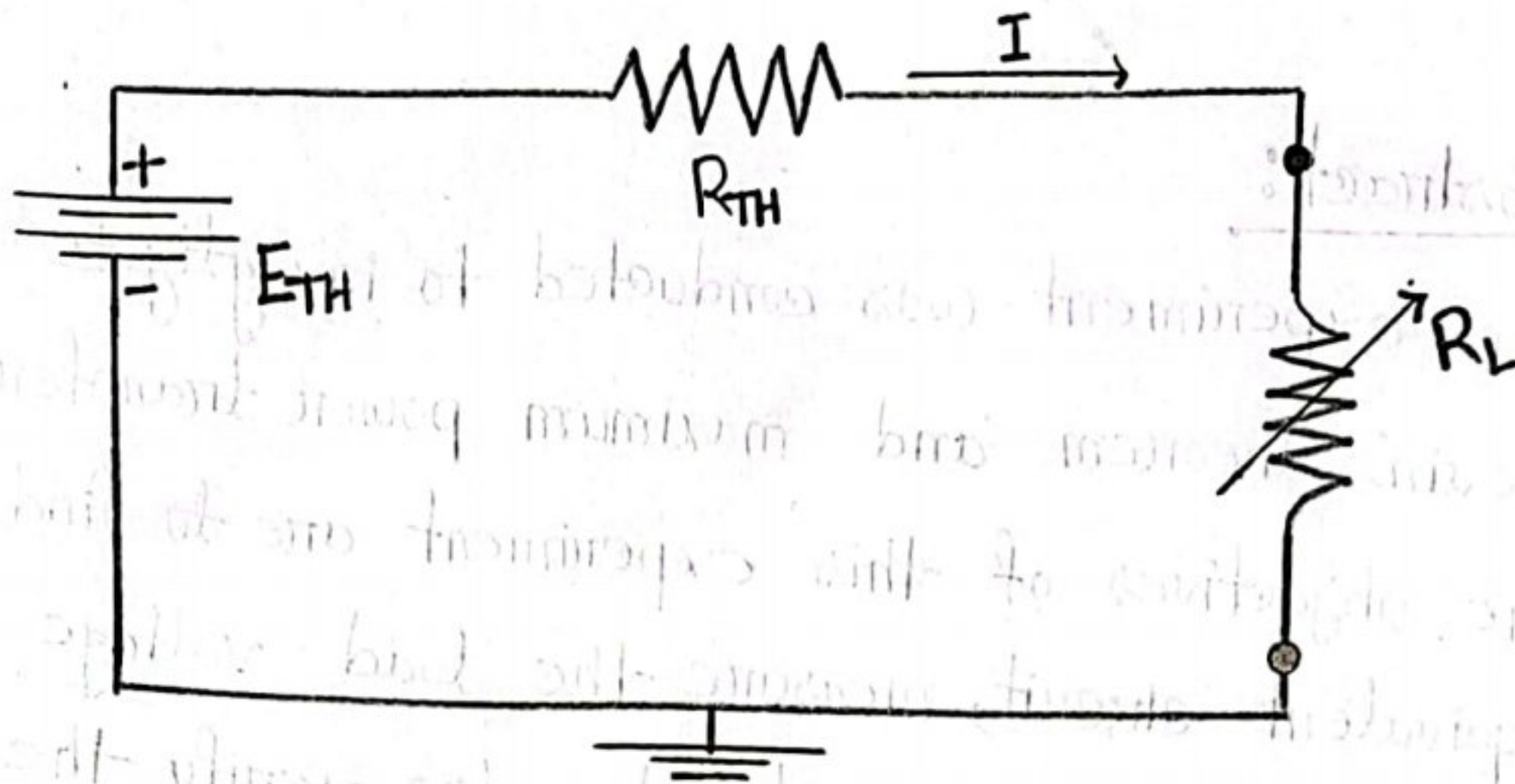


Figure 1: Thevenin's equivalent circuit

Maximum Power Transfer Theorem:

The maximum power transfer theorem states that, "A load will receive maximum power from a dc network when its total resistance is exactly equal to the Thevenin resistance of the network by the load."

For the Thevenin equivalent circuit (Figure 1), the maximum power will be delivered to the load when, $R_L = R_{TH}$. If the load resistance is lower or higher than the Thevenin resistance of the network, it will observe the less than the maximum power.

From Figure 1, the maximum power will be delivered to the load, when,

$$R_L = R_{TH}$$

$$\Rightarrow I_L = \frac{E_{TH}}{R_{TH} + R_L} = \frac{E_{TH}}{R_{TH} + R_{TH}} = \frac{E_{TH}}{2R_{TH}}$$

Now,

$$\text{power } P_L = I_L^2 R_L = \left(\frac{E_{TH}}{2R_{TH}} \right)^2 \times R_{TH}$$

$$= \frac{E_{TH}^2 R_{TH}}{4R_{TH}^2}$$

$$\Rightarrow P_{L \max} = \frac{E_{TH}^2}{4R_{TH}}$$

Circuit Diagram :

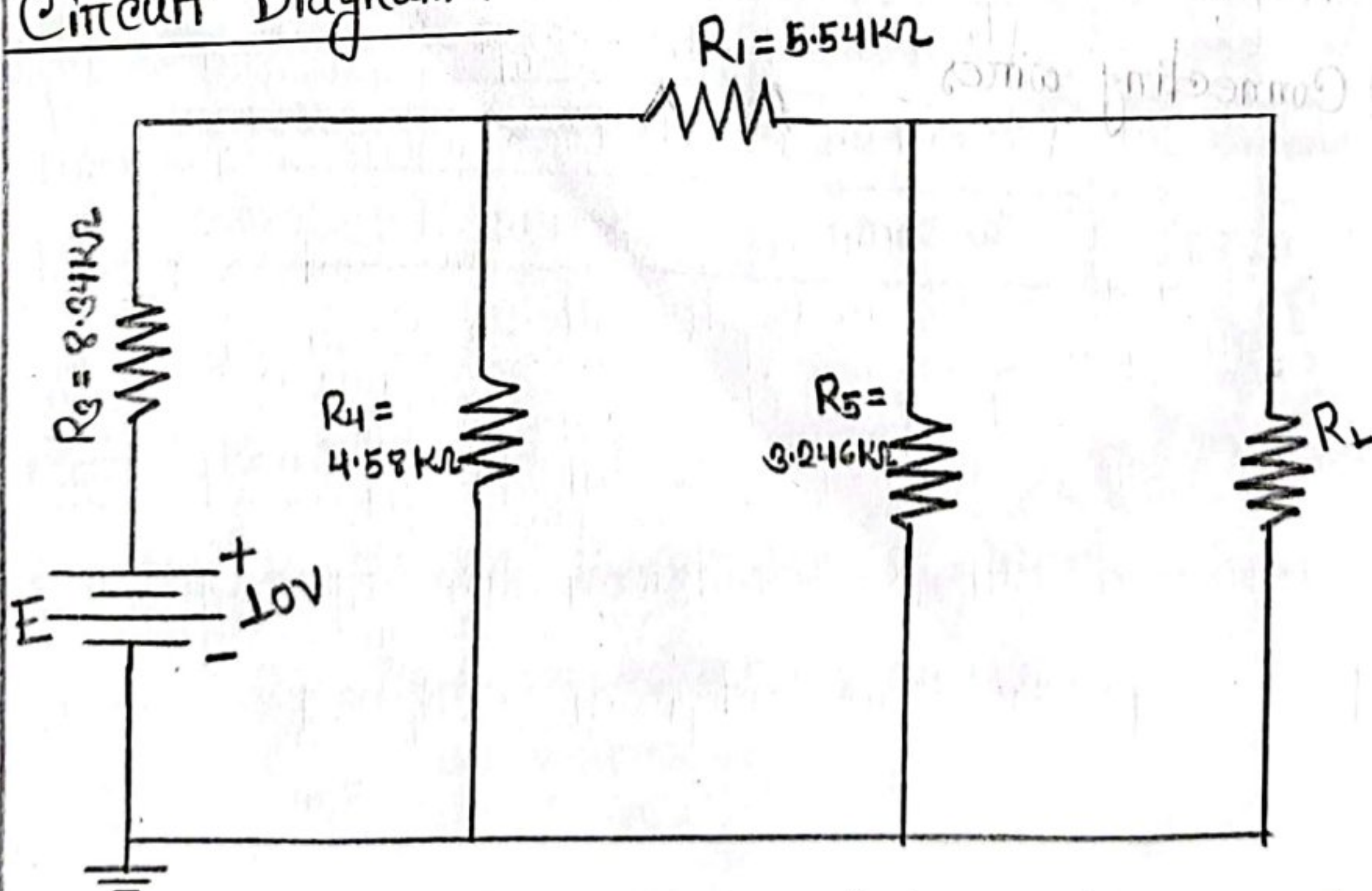


Figure 2: Series-Parallel circuit to apply Thevenin's Theorem.

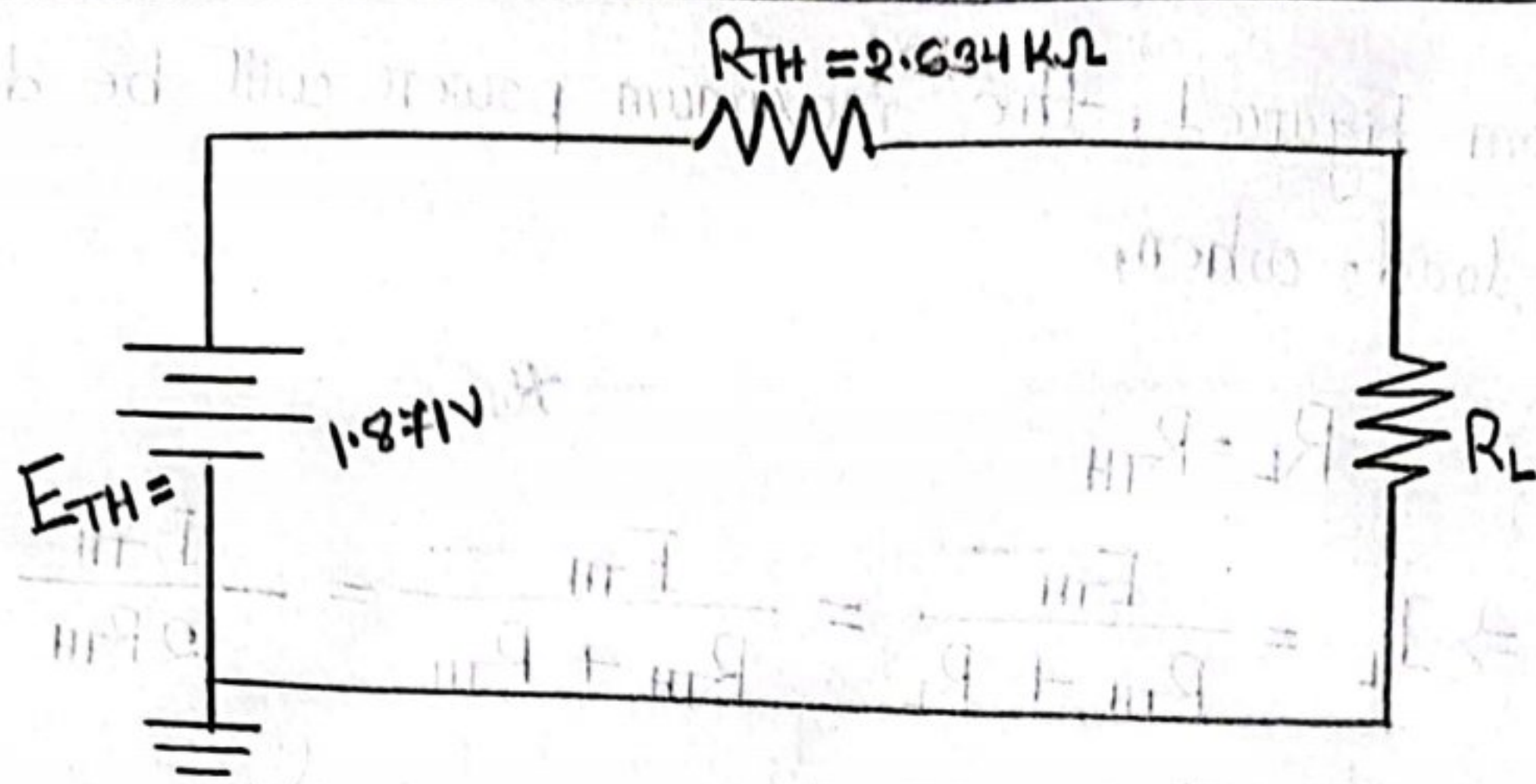


Figure-3 : Thevenin's equivalent circuit from figure-1.

List of Equipment:

- (i) Bread Board
- (ii) Digital multimeter
- (iii) Dc source
- (iv) Resistors
- (v) Connecting wires

Experimental Data:

Table-1 (For Thevinins Equivalent Circuit)

Thevinins Equivalent Voltage E_{TH}		Thevinins Equivalent Resistance R_{TH}	
Measured value	Calculated value	Measured value	Calculated value
1.871V	0.9802V	2.634 K Ω	2.212 K Ω

Table-2 (For Maximum Power Transfer Theorem)

R_L	V_L	I_L mA	P_L mW
0.634 K Ω	341 mV	0.538 mA	0.184 mW
1.634 K Ω	0.669V	0.41 mA	0.274 mW
2.634 K Ω	0.879V	0.334 mA	0.293 mW
3.634 K Ω	1.038V	0.286 mA	0.297 mW
4.634 K Ω	1.148V	0.248 mA	0.284 mW

Calculation:

For R_{TH} , $R_1 = 5.54 K\Omega$, $R_3 = 8.34 K\Omega$, $R_4 = 4.58 K\Omega$, $R_5 = 3.246 K\Omega$

$$R_{15} = (5.54 + 3.246) K\Omega = 8.786 K\Omega$$

$$R_{415} = \frac{4.58 \times 8.786 K\Omega}{4.58 + 8.786} = 3.011 K\Omega$$

$$R_{3415} = \frac{8.34 \times 3.011 K\Omega}{8.34 + 3.011} K\Omega = 2.212 K\Omega \quad \therefore R_{TH} = 2.212 K\Omega$$

For E_{TH} ,

$$R_{15} = 8.786 \text{ k}\Omega$$

$$R_{415} = 3.011 \text{ k}\Omega$$

$$R_{3415} = (8.34 + 3.011) \text{ k}\Omega$$


$$= 11.351 \text{ k}\Omega$$

Apply VDR,

$$V_{R_{415}} = \frac{R_{415}}{R_{3415}} \times 10\text{V}$$

$$= \frac{3.011}{11.351} \times 10\text{V}$$

$$= 2.653 \text{ V}$$

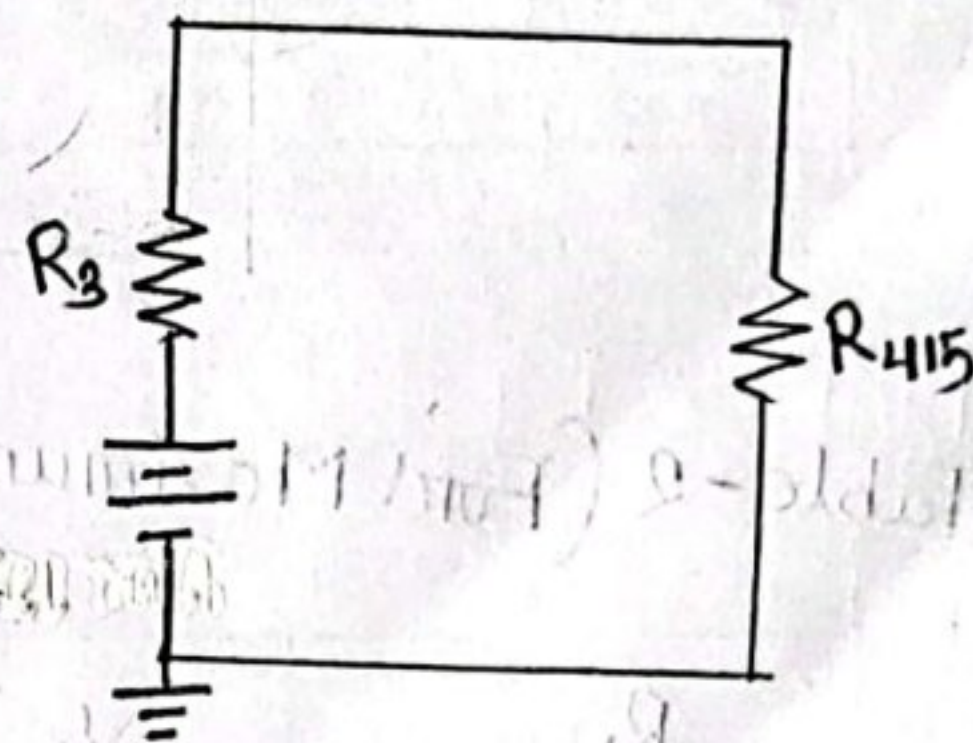



Again Apply VDR,

$$V_{R_5} = \frac{R_5}{R_{15}} \times V_{R_{415}}$$

$$= \frac{3.246}{8.786} \times 2.653$$

$$= 0.9802 \text{ V}$$

$$\therefore E_{TH} = 0.9802 \text{ V}$$

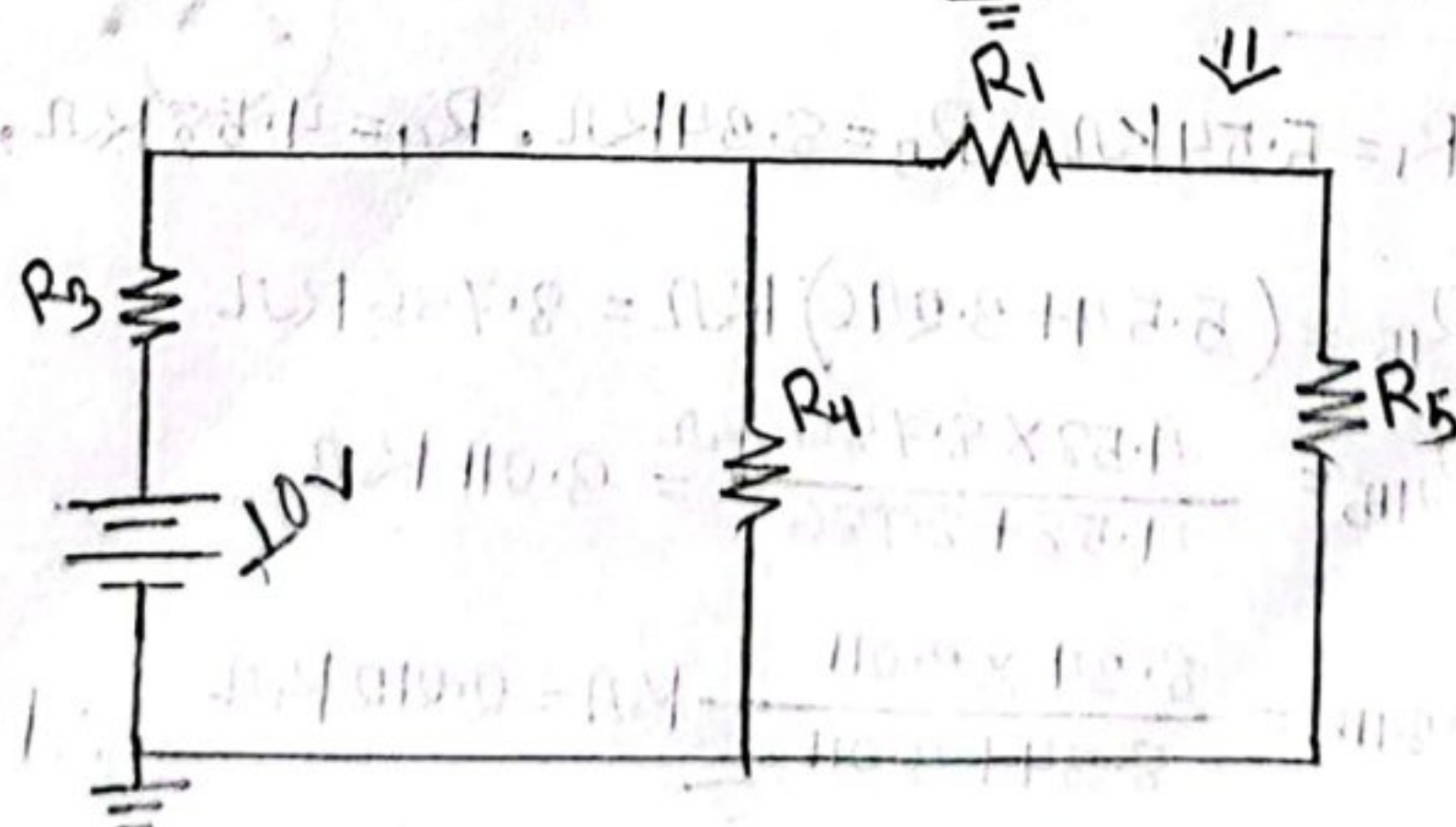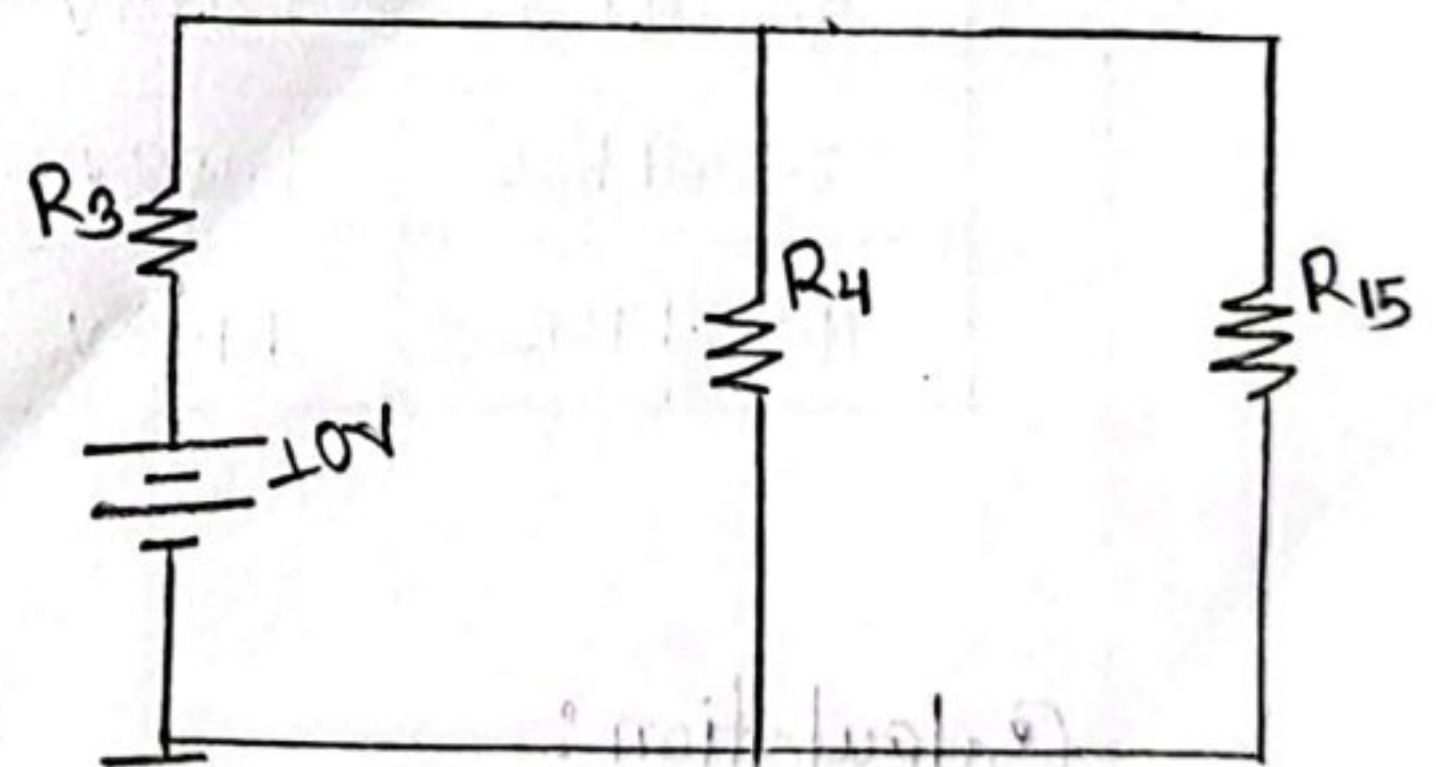

Discussion:

1. The bread board was checked before the start of the experiment.
2. The multimeter was checked also.
3. The value of the voltage was increased gradually as applying of a large voltage can damage the resistors.
4. The resistors was placed properly according to the figure.
5. Every data was measured carefully.
6. All the data was placed in the data table. carefully.
7. After the calculation by using the given equation a result was obtained.

Conclusion: The purpose of the experiment was to establish Thevins Theorem and Maximum Power Transfer Theorem. Conducting the experiment the objects we find Thevins equivalent circuit, the load voltage and load current from given network. After completing the experiment we are able to reducing complex circuit to an

equivalent circuit and from the calculation and result we find that a load receive maximum power when it's total resistance is exactly equal to the Thevinins resistance by the load from the network. So conducting the experiment we are able to verify the Thevinins Theorem and the Maximum power Theorem is also verified.

References:

i) Lab manual.

ii) Theory slides.